

**B.Tech. – VIEP – ELECTRONICS AND  
COMMUNICATION ENGINEERING (BTECVI)**

**Term-End Examination**

**December, 2017**

00409

**BIEL-019 : POWER ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

---


**Note :** *Attempt any seven questions. All questions carry equal marks. Use of scientific calculator is allowed. Missing data, if any, may be suitably assumed.*

---

1. (a) Explain the switching characteristics of power MOSFET. 5
- (b) Define  $di/dt$  and  $dv/dt$  rating of SCR. How is SCR protected against these ? 5
2. (a) Draw and explain the I – V characteristics of a Diac. Also write down some applications of a Diac. 5
- (b) What is Form Factor ? Evaluate the value of form factor for the half wave and full wave rectifiers. 5

3. With a circuit diagram, explain the operation of a three-phase full converter for constant load current. If the input to this circuit is three-phase, 50 Hz AC supply, determine the firing angle ( $\alpha$ ), for the SCR to obtain an output average DC voltage of 50% of the maximum. If the output voltage is 270 volts, calculate AC supply line and RMS line voltage. 10
4. (a) Discuss the effect of source inductance on the performance of a single phase full converter. 5
- (b) Explain the working of a voltage commutated chopper with the help of a circuit diagram and waveforms. 5
5. (a) Describe the operating principle of a chopper with necessary diagram. 4
- (b) The DC chopper shown in Figure 1 has a resistive load of  $R = 10 \Omega$  and the input DC voltage  $V = 200$  volts. When the chopper switch remains ON, its voltage drop is 2 volts and the chopper frequency is 1 kHz. If the duty cycle is 30%, determine : 6
- (i) The average load voltage

- (ii) RMS load voltage
- (iii) Form factor and Ripple factor

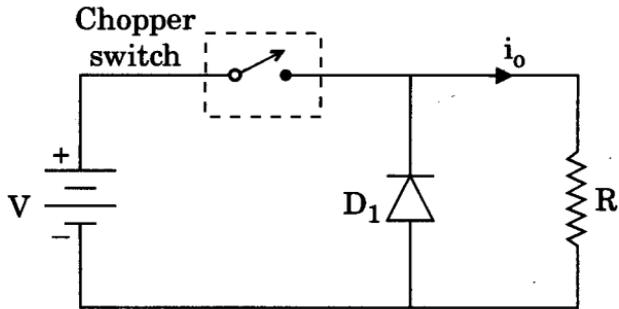

*Figure 1*

6. Draw and explain the operation of single-phase half-bridge voltage source inverters with their steady state analysis. 10
7. (a) Why are thyristors not preferred for inverters ? Write down the various performance parameters of inverters. 5  
 (b) What are the advantages of PWM control in inverters ? Compare half-bridge and full-bridge inverters. 5
8. Describe the operation of separately excited drives for the single phase with necessary diagrams and waveforms. 10
9. Draw and explain the operating principle of an induction motor with its characteristics. How is it different from a DC motor ? 10

**10.** Write short notes on any **two** of the following : *2×5=10*

- (a) Slip Power Recovery Scheme of Induction Motors
  - (b) Modified McMurray Half-Bridge Inverter
  - (c) Dual Converters
-