

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)**

Term-End Examination

December, 2018

00473

BIELE-004 : RF CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. Missing data may be suitably assumed. All questions carry equal marks.

1. (a) Discuss briefly the importance of radio frequency design. 5
- (b) Determine the radius of the AWG 26 wire, if the diameter of the AWG 50 wire is 1.0 mil (or 2.54×10^{-5} m). 5

2. (a) What is high frequency resistor ? Draw electric equivalent circuit representation for a high frequency wire wound resistor. 5
- (b) Discuss Transmission line theory. Also plot voltage distribution as a function of time and space. 5

- 3.- Derive voltage and current equation of the parallel plate transmission line. 10
4. (a) Discuss classical two-port noise theory in RF design. 5
- (b) Briefly discuss low frequency hybrid network description of a BJT. 5
5. (a) Explain the key parameters of RF amplifier in terms of performance specification. 5
- (b) With the help of block diagram, explain the key characteristics of mixers. 5
6. (a) Explain the feedback oscillator design on the basis of Pi-type feedback. 5
- (b) Discuss heterodyne receiver system incorporating a mixer. 5
7. Define the following terms with mathematical expression : $4+4+2=10$
- (a) Intrinsic wave impedance
- (b) Phase velocity
- (c) Wavelength

8. Write short notes on any **two** of the following : $5+5=10$
- (a) LNA
 - (b) Class A Power Amplifier
 - (c) Modulation of Power Amplifiers
9. Explain the stability criteria of power amplifier. Also derive input stability and output stability circle equation. 10
10. Discuss the design steps for low frequency Colpitts oscillator using h-parameters. 10
-