

**B.Tech. - VIEP - ELECTRICAL ENGINEERING
(BTELVI)**

00443

Term-End Examination

December, 2018

BIEE-024 : POWER ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. All questions carry equal marks. Use of scientific calculator is permitted. Assume suitable data, wherever not provided.

1. Discuss the turn-on and turn-off techniques of thyristor. 10
2. Describe the working of a single-phase half converter with RL load. Draw the waveform of supply voltage, load voltage, load current and voltage across the thyristor. 10
3. With suitable waveforms, discuss UJT triggering circuit for thyristor. 10
4. Describe a step-up chopper with relevant current and voltage waveforms as a function of time. 10

5. A step-down chopper, fed from 220 V dc is connected to RL load with $R = 10 \Omega$ and $L = 150 \text{ mH}$. Chopper frequency is 1250 Hz and duty cycle is 0.5. Calculate 10
- (a) Maximum and minimum voltage of load current,
 - (b) Maximum value of ripple current,
 - (c) Average and RMS values of load current,
 - (d) RMS value of chopper current.
6. With a neat circuit diagram, explain the working of voltage source inverter. 10
7. Discuss the working principle of single-phase to single-phase step-down cycloconverter with the help of bridge type configurations. 10
8. What is commutation ? Discuss the operation of complementary commutation with the help of neat circuit and relevant waveforms. 10
9. Explain the working of three-phase inverter for 120° mode of conduction. Draw the corresponding waveforms. 10

10. Write short notes on any *two* of the following : 2×5=10

- (a) VI characteristics of MOS controlled thyristor
 - (b) GTO
 - (c) Scrubber circuit for the protection of SCR
 - (d) Switching characteristics of power transistor
-