

**DIPLOMA IN MECHANICAL ENGINEERING
(DME)**

Term-End Examination

00103 December, 2018

BEE-031 : ELECTRICAL TECHNOLOGY

Time : 2 hours

Maximum Marks : 70

Note : Attempt *five* questions in all, including question no. 1 which is **compulsory**. Use of scientific calculator is permitted.

1. (a) Write *True* or *False* for the following statements : $7 \times 1 = 7$
- (i) As per Kirchhoff's Voltage Law (KVL), the sum of voltages in closed network is zero at any instant of time.
 - (ii) The efficiency of maximum power transfer theorem is 93%.
 - (iii) DC series motor has highest starting torque.
 - (iv) Transformer is used to step up or step down the frequency.
 - (v) Induction motor runs at constant speed.
 - (vi) Single-phase induction motor is a self-starting motor.
 - (vii) Synchronous motor operates for lagging power factor only.

(b) Fill in the blanks :

7×1=7

- (i) As per KCL, algebraic sum of _____ is zero at a node.
- (ii) The output and input relation of linear element always follows _____ and homogeneity principles.
- (iii) In case of star connection, line voltage is equal to _____ times the phase voltage.
- (iv) Effect of armature flux on the main field flux is called _____ .
- (v) No load current is _____ of rated current in case of transformer.
- (vi) For induction motor, Rotor Copper loss = _____ × Rotor input.
- (vii) _____ motor can be used as a synchronous condenser.

2. (a) Draw the phasor diagrams for the following :

8

- (i) RL circuit
- (ii) RC circuit
- (iii) RLC series circuit
- (iv) RLC parallel circuit

(b) Why is three phase system preferred over single phase system ? Explain. 6

3. (a) State and prove maximum power transfer theorem. 8

(b) Calculate current I as shown in Figure 1. 6

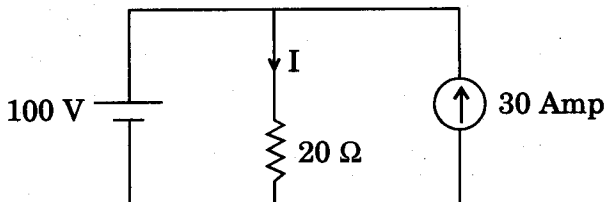


Figure 1

4. (a) Explain functions of the following parts of dc machine : 7

(i) Field system

(ii) Armature

(b) Explain internal and external curves for separately excited DC generator. 7

5. (a) Describe torque-slip curve of three-phase induction motor. 7

(b) A 3-phase induction motor has 2 poles and is connected to 400 V, 50 Hz supply. Calculate the actual rotor speed and rotor frequency when the slip is 4%. 7

6. (a) What are the differences between a synchronous motor and an induction motor? 7
- (b) Explain three-point starter with neat schematic diagram. 7
7. Write short notes on any *two* of the following: $2 \times 7 = 14$
- (a) Speed Control of DC Series Motor
- (b) Auto Transformer
- (c) Hunting and Damper Winding
-