

**B.Tech. - VIEP - ELECTRICAL ENGINEERING
(BTELVI)**

Term-End Examination

00323

December, 2018

BIEEE-012 : ACTIVE FILTER DESIGN

Time : 3 hours

Maximum Marks : 70

*Note : Attempt any **seven** questions. All questions carry equal marks. Use of scientific calculator is permitted. Missing data may be suitably assumed.*

1. A maximally flat magnitude transfer function is the Butterworth approximation. Prove that its poles lie on a unit circle. 10
2. Prove that the poles for Chebyshev function lie on an ellipse. 10
3. Draw the ideal and practical frequency response curves for the five filter functions. 10
4. Discuss Antoniou Gytrators. Realise various filters using Antoniou Gytrators. 5+5=10
5. Draw and explain the use of bridged T network in active filters. 10

6. Draw the circuit diagram of a KHN Biquad. Derive the transfer functions and hence the filter parameters. 10
7. Draw the circuit diagram of Tow-Thomas Biquad. Derive its transfer function and hence the filter parameters. 10
8. Transform a second order passive RLC high pass filter circuit into an active RC filter using Antoniou Gyration. 10
9. Describe how Q enhancement technique is achieved in filters. What is pole frequency error problem? 10
10. Write short notes on any **two** of the following : $2 \times 5 = 10$
- (a) Bessel's Approximation
 - (b) Phase and Group Delay
 - (c) Switched-Capacitor Filters
 - (d) Elementary Ideas of Compensation
-