

1450071

No. of Printed Pages : 4

**BEE-042**

**DIPLOMA IN MECHANICAL  
ENGINEERING (DME)**

**Term-End Examination**

**December, 2019**

**BEE-042 : ELECTRONICS**

*Time : 2 Hours*

*Maximum Marks : 70*

---

*Note : Question No. 1 is compulsory. Attempt five questions in all. Use of scientific calculator is permitted.*

---

---

1. State True or False for the following questions :

7×2=14

- (a) A Zener diode utilizes forward characteristics for its operation.
- (b) The most commonly used transistor configuration is common emitter configuration.
- (c) SCR is a bidirectional device.

- (d) The binary number 10101 is equivalent to decimal number 21.
  - (e) A flip-flop can store binary information.
  - (f) An insulator has a large 'forbidden energy gap'.
  - (g) BJT can be used as a switch.
2. (a) Draw and explain full wave bridge rectifier. 7
- (b) Explain, how Zener diode maintains constant voltage across the load. 7
3. (a) Compare the salient features of a PNP-type transistor with that of a NPN-type transistor. 7
- (b) Describe the operation of half adder. Also, write its truth table. 7
4. (a) Explain the construction and working of TRIAC. Also, draw its I-V characteristics. 8

- (b) Explain the following static performance parameters : 6
- (i) Accuracy
  - (ii) Sensitivity
  - (iii) Drift
5. (a) What is a transducer ? Classify different transducers. 7
- (b) What is a digital voltmeter ? Discuss the various types of digital voltmeter. 7
6. (a) With the help of block diagram, explain construction and working of a strip chart recorder. 7
- (b) Explain clamper with its circuit diagram. Also, draw its input and output voltage wave form. 7

7. Write short notes on any *two* of the following : 7 each

(a) Microcomputer

(b) AM Radio Receiver

(c) RVDT (Rotary Variable Differential Transducer)