

**B.Tech. ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

June, 2012

BIEL-003 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : *Attempt any seven questions. All questions carry equal marks.*

1. (a) Design NAND gate using CMOS and Explain it. 5
- (b) Differentiate between ROM, PLA and PAL. 5
2. (a) Design a 4-digit 7-segment LED display system with leading zero blanking 6
- (b) Construct Hamming code for BCD data 0110. Use even parity. 4
3. (a) Make K-Map for the following function 5
 $f = AB + A\bar{C} + C + AD + A\bar{B}C + ABC$
Express f in canonical SOP form and Minimize it. Realize the minimized expression using NAND gates only.
- (b) Design JK flip-flop. Explain Race Around condition in JK flip-flop. 5

4. Draw TTL circuit for Totempole output and explain its working. Why it is not used for WIRED AND connection. **10**
5. (a) Explain Quine-Mc-cluskey method and differentiate between Prime Implicant and Essential Prime Implicant. **6**
- (b) Write and Explain Excitation table for D flip-flop. **4**
6. Design a digital system with two flip-flops E and F and one 4-bit binary counter, A the individual flip-flop's in A are denoted by A_4, A_3, A_2, A_1 with A_4 holding the MSB of the count. A start signal S initiates the system operation by clearing the counter A and flip-flop F. The counter then incremented by 1 starting from next clock pulse and continues to increment until operation stop Counter bits A_3 and A_4 determine sequence of operations:
- If $A_3=0$, $E \leftarrow 0$ and count continues.
- If $A_3=1$, $E \leftarrow 1$ and then if $A_4=0$, count continues but if $A_4=1$, $F \leftarrow 1$ on next clock pulse and system stops counting. Draw the ASM chart for the system.
7. (a) Draw the circuit of 4-bit ring counter and explain its operation. Write its applications. **5**
- (b) What is the difference between static RAM and Dynamic RAM. **5**

8. (a) Implement with 8 : 1 Mux 5
 $F(A, B, C, D) = \Sigma m(0, 1, 3, 4, 7, 8, 9, 11, 14, 15)$
- (b) Realize the J-K flip flop using SR flip flop. 5
9. (a) Design a Decade synchronous up counter. 5
Use JK flip-flop.
- (b) Why Asynchronous counters are called 5
Ripple counters ? Explain.
10. Write short note on *any two* of the following : 5x2=10
- (a) Flash Memory
- (b) MOS as a switch.
- (c) ASCII and ESCII codes.
-