## No. of Printed Pages : 2

01595

**BIEE-004** 

# B.Tech. VIEP - ELECTRICAL ENGINEERING - III / BTELVI

#### **Term-End Examination**

## June, 2012

# **BIEE-004 : ELECTRICAL MACHINE-I**

Time : 3 Hours		Hours Max	Maximum Marks : 70	
Not	te: A U F	Attempt <i>any seven</i> questions. Jes of non-programmable scient permitted.	ific calculator is	
1.	(a) (b)	What is armature reaction ? D effects of armature reaction on th of d.c. machines . How the reaction is minimized ? Define commutation. Explain the commutation in d.c. generators sketches.	escribe the e operation armature 2x5=10 e process of with neat	
2.	(a) (b)	Derive the torque equation of a Explain the principal of operat machine.	d.c. motor. ion of d.c. <b>2x5=10</b>	
3.	A 110 V d.c. shunt generator delivers a load current of 50 A. The armature resistance is 0.2 $\Omega$ and the field circuit resistance is 55 $\Omega$ . The generator, rotating at a speed of 1800 r.p.m; has 6 poles, lap wound, and a total of 360 conductors Calculate the no-load voltage at the armature and the flux per pole.		ers a load 10 ce is $0.2 \Omega$ , $5 \Omega$ . The r.p.m; has onductors. nature and	

**BIEE-004** 

1

P.T.O.

- 4. A 250 V d.c. shunt motor having an armature 10 resistance of 0.25  $\Omega$  carries an armature current of 50 A and runs at 750 r.p.m. If the flux is reduced by 10%. Find the speed. Assume that the load torque remains the same.
- Explain the speed-armature current, torque 10 current and speed-torque characteristics of d.c. series motor.
- 6. Explain the necessity of starter in a d.c. motor and describe a three-point-starter with a neat sketch.
- 7. Describe Swinburne's test with the help of a neat 10 diagram to find out the efficiency of a d.c. machine. What are main advantage and disadvantages of this test ?
- 8. (a) Describe the various losses in a single phase transformer. 2x5=10
  - (b) What is an auto transformer ? State its merits and demerits over the two winding transformer.
- 9. Describe the construction, working, types, 10 connections of three phase transformer.
- 10. Write short notes on *any two* of the following : 2x5=10
  - (a) Speed control of d.c. motor.
  - (b) Power transformer
  - (c) Regenerative braking in d.c. series motor.

**BIEE-004** 

2