

DECVI/DELVI/DCSVI/ACECVI/ACELVI/  
ACSVI

Term-End Examination

June, 2012

02120

BIEL-027 : APPLIED ELECTRONICS

Time : 2 Hours

Maximum Marks : 70

- 
- Note :** (1) Question No. 1 is *compulsory*.  
(2) Attempt *any five* questions.  
(3) Each question carry *equal* marks.  
(4) Use of scientific calculator is *allowed*.  
(5) Answer must be given in English only.
- 

1. This question contains fill in the blanks, and objective type questions. 7x2=14
- (a) Tuned amplifiers are generally not used in : 2
- (i) TV receivers
  - (ii) Radio receivers
  - (iii) Public address systems
  - (iv) Radar receivers
- (b) To increase the bandwidth, the distributed 2  
amplifier uses \_\_\_\_\_.
- (c) A monostable multivibrator has : 2
- (i) two stable states
  - (ii) one stable states
  - (iii) no stable states
  - (iv) two quasi stable states

- (d) Crystal oscillator uses \_\_\_\_\_. 2
- (e) Transfer gain  $A_f$  of a feed back amplifier is given by \_\_\_\_\_. 2
- (f) The maximum theoretical collector circuit efficiency of class B amplifier is 2
- (i) 15%           (ii) 25%
- (iii) 50%         (iv) 78.5%
- (g) In a class AB amplifier with sinusoidal input signal, the output current flows for \_\_\_\_\_. 2
2. (a) Explain how is FET used as a Voltage Variable Resistance (VVR) ? Define 7
- (i) transconductance  $g_m$
- (ii) drain resistance  $r_d$
- (b) How are the power amplifiers classified ? 7
- Explain each type. Draw the circuit diagram of a Class AB push - pull amplifier with its working.
3. (a) Explain the working of a Wein - bridge oscillator. Derive an expression for the frequency of oscillation. What are the merits and demerits of this oscillator ? 7
- (b) Explain the effect of negative feedback on 7
- (i) gain and stability
- (ii) distortion of an amplifier

4. (a) Explain the working of UJT as relaxation oscillator. Give their application. 7
- (b) Draw the block diagram of CRO, and explain the function of time base generator and Trigger circuit of CRO. 7
5. (a) Sketch  $I_R$  and  $V_o$  w.r.t time for the n/w shown in figure (1) for the input  $V_i$  shown in the same figure. Assume that both diodes are silicon type  $R_f = 0\Omega$  and  $R_r = \infty$  with  $V_f = 0.7V$ . 7

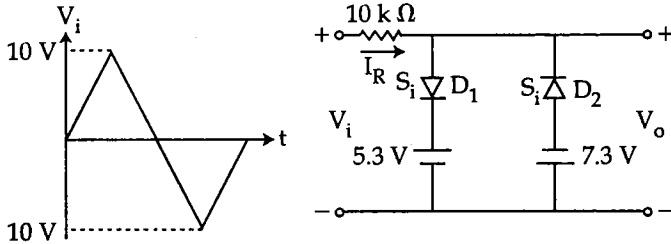


Figure (1)

- (b) Determine output voltage  $V_o$  for the circuit shown in figure (2) for the i/p signal shown in same figure. 7

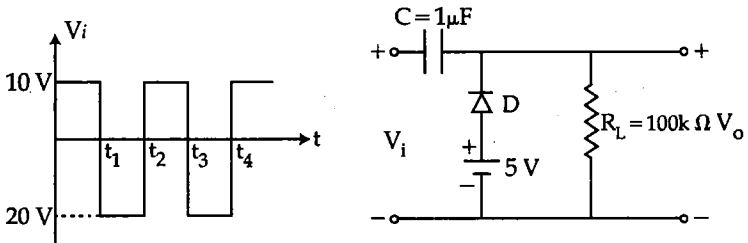


Figure (2)

6. (a) What is the need for trouble shooting ? 7  
Explain the important steps for testing.
- (b) Derive the input resistance and o/p resistance of current series feedback. 7
7. (a) Draw and explain the working of Monostable Multivibrator. Give its specific application. 7
- (b) Consider the class B amplifier of figure (3) 7  
with  $R_L = 16\Omega$  and  $V_{CC} = 12V$ . If the i/p ac signal produces a peak voltage o/p of  $V_m = 6V$  across the load resistor  $R_L$ , find the i/p power, o/p power, amplifier efficiency and power dissipated by the transistor.

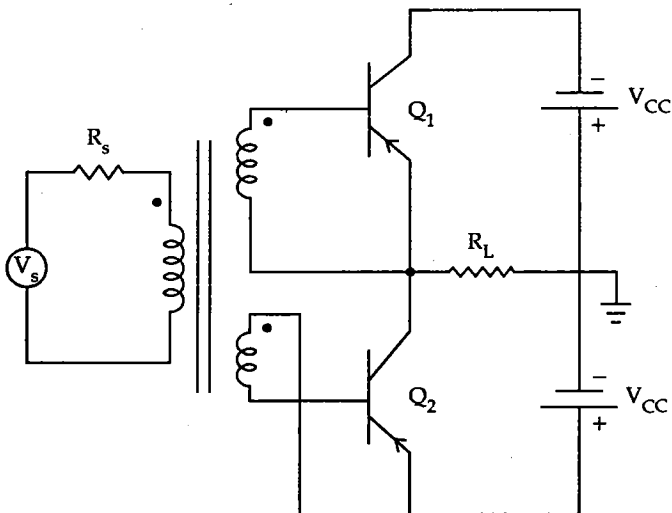


Figure (3)

8. Write short note on *any four* of the following :  $3.5 \times 4 = 14$

- (a) Classification of feedback
  - (b) Barkhausen criterion
  - (c) Hartley Oscillator
  - (d) Miller sweep generator
  - (e) Enhancement type MOSFET
  - (f) Active testing.
-