

**DIPLOMA IN - ELECTRICAL ENGINEERING**

**Term-End Examination**

**June, 2012**

**BIEE-033 : ELECTRICAL CIRCUIT THEORY**

*Time : 2 Hours*

*Maximum Marks : 70*


---

*Note : All the questions are to be answered in English only. Question no. 1 is compulsory. Any four questions are to be attempted out of question 2 to 8. Use of calculator is allowed.*


---

1. Write *True* or *False* in Question No (1) :
- (a) There is no relation between Thevenin's theorem and Norton's theorem. 2
  - (b) A current source has internal impedance connection in series with it. 2
  - (c) Q-factor of a coil is reciprocal to power factor of a coil. 2
  - (d) A parallel resonance LC circuit in series with load is a band pass-filter. 2
  - (e) In R-L-C circuit voltage across the resistance at resonance frequency is equal to applied voltage. 2
  - (f) If power factor of circuit is unity, the reactive power is zero. 2
  - (g) At very low frequency a parallel R-C behaves as almost pure capacitive circuit. 2

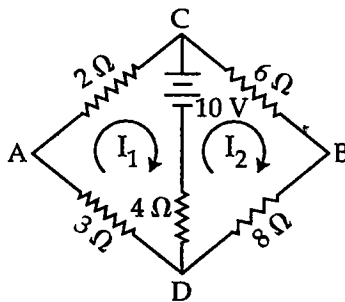2. (a) What is active and passive Elements. What are independent Voltage source and independent Current Source. 7
- (b) Derive the formula for current in Parallel circuits (Current division formula) 7
3. (a) Derive formula for Star to Delta transformation. 7
- (b) Explain Thevenin's theorem. With diagram and steps to find Thevenin equivalent. 7
4. (a) Find currents in different branches, current supplied by battery and Potential difference between A and B. 7



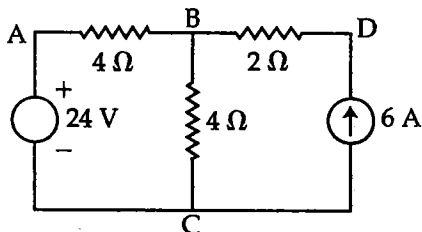- (b) Use Superposition theorem to find currents in various branches of the circuit. 7



5. (a) What is parallel Resonance. Derive the formula for frequency and Quality factor. 7
- (b) A coil of inductance 0.75H and resistance 400 Ohm is a part of a series resonant circuit having a resonant frequency of 55 Hz. If the supply is 250 V, 50 Hz find
- (i) Current (ii) Power factor
- (iii) Voltage across coil
6. (a) State with diagram. How will you measure Power of 3 phase circuit by two Wattmeter method. 7
- (b) Derive the formula for Bandwidth and Quality factor for series resonance circuit. 7
7. (a) Define Power factor. Active Power, Reactive Power and Apparent Power in A.C circuit. 7
- (b) Define and write formula for Impedance Parameter for two port network 7
8. Attempt *any four* and write short answer :  $3.5 \times 4 = 14$
- (a) Poles and Zero in Networks.
- (b) Kirchhoff's Laws
- (c) Mesh and Nodal Analysis
- (d) Network Synthesis
- (e) Lumped Networks
- (f) Source Transformation
-