

**B.Tech. ELECTRONICS AND  
COMMUNICATION ENGINEERING (BTECVI)**

**Term-End Examination**

**June, 2013**

**BIEL-019 : POWER ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

**Note :** (i) *Attempt any seven questions.*

(ii) *All questions carry equal marks.*

- 
- |    |     |  |    |
|----|-----|--|----|
| 1. | (a) | Define holding current.  | 2  |
|    | (b) | How can a thyristor turned off ?   | 2  |
|    | (c) | How is inverter circuit classified based on commutation circuitry ?  | 3  |
|    | (d) | What are the applications of Series inverter ?   | 3  |
| 2. | (a) | Draw the static V - I characteristics of SCR and explain its modes of operation.   | 5  |
|    | (b) | Define di/dt and dv/dt ratings of SCR. How is SCR protected against these ?  | 5  |
| 3. |     | A three phase full converter is fed by 400 volts, three phase, 50 Hz supply. The average load current is 150 A and load is highly inductive. For a firing angle of 60 degrees, find output power, average, rms and peak current through thyristors and peak inverse voltage. | 10 |

4. What are dual converters ? Explain operation of a three phase dual converter using circulating current mode of operation. How are firing angles of two converters controlled ? 10
5. Describe the principle of step - up chopper. Derive an expression for the average output voltage in terms of input dc voltages and duty cycle. 10
6. Describe the operation of series inverter with aid of diagrams. Describe an expression for output frequency, current and voltages. What are the advantages of basic series inverter ? 10
7. Explain briefly the characteristics and principle of operation of Induction motor. 10
8. Describe in detail "Single - Phase separately Excited drives" and "Single - Phase Series Motor Drives". 10
9. Explain the operation of 3 phase bridge inverter for 120° degree mode of operation with aid of relevant phase and line voltage waveforms. 10
10. Write short notes on *any two* of the following : 2x5=10
  - (a) Variable frequency control
  - (b) Single phase PWM Inverters
  - (c) DC chopper Drives