

**DIPLOMA VIEP ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)/
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination 00001

June, 2013

BIEL-028 : CIRCUITS AND NETWORKS

Time : 2 hours

Maximum Marks : 70

-
- Note :** (i) Attempt five questions in all.
(ii) Question No. 1 is compulsory.
(iii) Use of scientific calculator is permitted.
-

1. Mention true or false for the statement given below. 2x7=14
- (a) If same current passes through each resistor of a combination, they must be connected in parallel.
 - (b) The impedance of a series RL circuit is given by the algebraic sum of R and x_L .
 - (c) Greater the Bandwidth, higher the selectivity.
 - (d) Given poles and zeros, the network function can be determined.
 - (e) A tuned circuit is a resonant circuit.
 - (f) A Band pass filter can be converted into a bandstop filter simply by interchanging its resonant circuits.

- (g) Laplace transform is used to convert time domain signal to frequency domain signal.
2. (a) Determine the current through 10Ω resistor for the circuit shown in fig (i). **2x7=14**

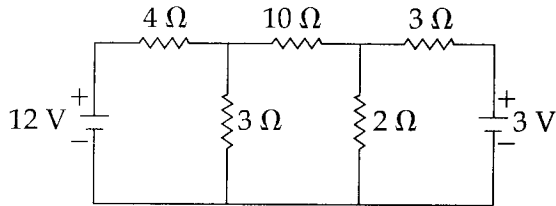


Fig. (i)

- (b) Find the current i using superposition theorem for the circuit shown in fig (ii).

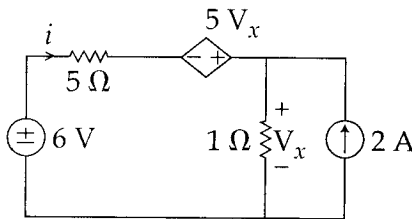


Fig. (ii)

3. For a parallel resonant circuit shown in fig (iii), **14**
- Find the resonant frequency
 - Q of the circuit
 - Bandwidth
 - Circuit impedance at resonance

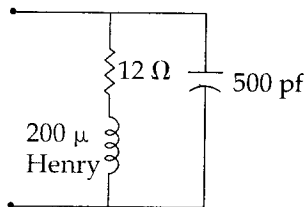


Fig. (iii)

4. (a) The RC network shown in fig (iv) acts as a low pass filter. Derive expression for cut off frequency and find the value of 'C' If $R = 2 \text{ k}\Omega$, and $f_c = 800 \text{ Hz}$? $2 \times 7 = 14$

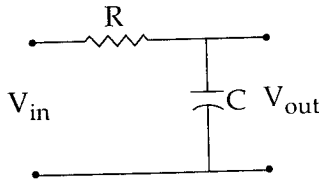


Fig. (iv)

- (b) Derive the reciprocity condition for y-parameter.

5. (a) Derive z - parameter of the network shown in fig (v). $2 \times 7 = 14$

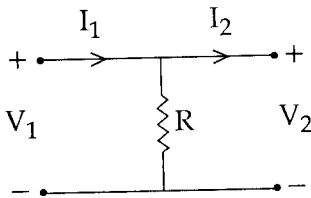


Fig. (v)

- (b) Two identical sections of the network shown in fig (vi) are connected in parallel. Calculate the Y-parameters of the resulting network.

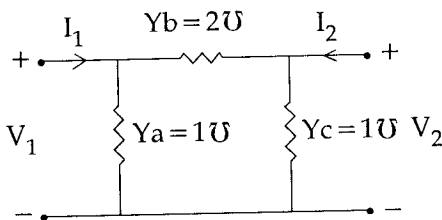


Fig. (vi)

6. (a) Discuss the natural response of RC series network. 2x7=14

(b) The network shown in fig (vii) is in steady state with the switch k closed. At $t=0$, the switch is opened. Determine the voltage across the switch V_k at $t=0^+$.

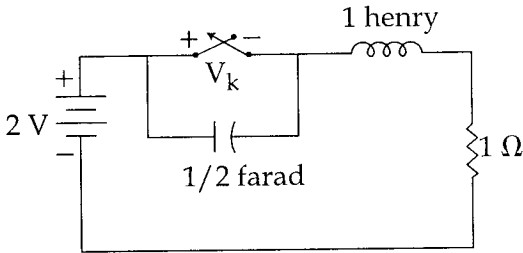


Fig. (vii)

7. (a) For the network shown in fig (viii) find transfer admittance $Y_{12}(s)$ and plot the poles and zeros of the function. 10

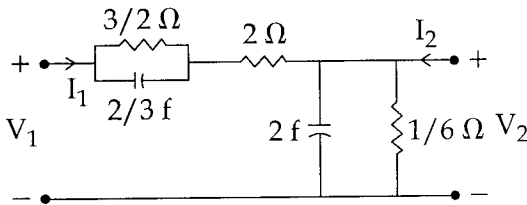


Fig. (viii)

(b) State the significance of poles and zeros. 4

8. Write short notes on *any four* :

4x3.5=14

- (a) Composite low pass filter
 - (b) Iterative impedance
 - (c) Inter relation between z and h parameters.
 - (d) Series resonance
 - (e) Constant K type band stop filter.
-