

**DIPLOMA IN ELECTRICAL ENGINEERING
(DELVI)/ADVANCED LEVEL CERTIFICATE
COURSE IN ELECTRICAL ENGINEERING
(ACELVI)**

Term-End Examination

June, 2013

**BIEE-030 : INDUSTRIAL DRIVES AND
CONTROLS**

Time : 2 hours

Maximum Marks : 70

-
- Note :** (i) Attempt *any five* questions.
(ii) Question No. 1 is *compulsory*. (objective type)
(iii) Draw neat and clean diagram, if any, required.
-

1. (a) In a thyristor, the holding current I_H is : $7 \times 2 = 14$
- (i) more than the Catching current I_L
 - (ii) less than I_L
 - (iii) equal to I_L
 - (iv) equal to zero
- (b) A triac is a :
- (i) 2 terminal switch
 - (ii) 2 terminal bilateral switch
 - (iii) 3 terminal unilateral switch
 - (iv) 3 terminal bidirection switch

- (c) A four quadrant chopper cannot be operated as :
- (i) One quadrant chopper
 - (ii) Cycloconverter
 - (iii) Inverter
 - (iv) bi - directional rectifier
- (d) The most suitable device for high frequency inversion in SMPS is :
- (i) BJT
 - (ii) IGBT
 - (iii) MOSFET
 - (iv) GTO
- (e) The most suitable solid state converter for controlling the speed of the three - phase cage motor at 25 Hz is :
- (i) Cycloconverter
 - (ii) CSI
 - (iii) VSI
 - (iv) Load Commutated Converter
- (f) In a thyristor controlled rectifier the Firing angle of thyristor is to be controlled in the range of :
- (i) 0 to 90°
 - (ii) 0 to 180°
 - (iii) 90 to 180°
 - (iv) 90 to 270°
- (g) In case of VSI, FD can be avoided for the load of :
- (i) Inductive nature
 - (ii) Capacitive nature
 - (iii) Resistive nature
 - (iv) Back emf nature

2. (a) Explain with neat waveform for speed control of dc motor using single phase fully controlled rectifier. 7
- (b) Draw speed - torque characteristics of dc shunt motor and derive relation between firing angle and speed. 7
3. (a) Explain single phase half wave and semiconverter drive for dc series motor control. 7
- (b) Draw the waveform of output voltage and current for single phase semi - converter connected with separately excited dc motor. 7
4. (a) Explain difference between single phase and three phase fully controlled drive connected to dc shunt motor with neat waveform. 7
- (b) Draw the output voltage and current waveform of 3 phase semi-converter drive. 7
5. (a) Explain chopper drive connected to DC motor and derive the relation between duty cycle and speed. 7
- (b) Draw continuous and discontinuous waveform of single and four quadrant chopper drive. 7

6. (a) What are draw backs of SCR over TCR, also explain advantage of thyristor power converters. 7
- (b) What do you understand by the dv/dt rating of a thyristor ? 7
7. (a) Explain PWM control in detail : 7
- (b) Explain v/f control of induction motor. 7
8. (a) Compare VSI and CSI. 7
- (b) Explain with waveform cycloconverter drive. 7
-