

**DIPLOMA IN ELECTRICAL ENGINEERING  
(DELVI)**

**Term-End Examination**

**June, 2013**

**BIEE-033 : ELECTRICAL CIRCUIT THEORY**

*Time : 2 hours*

*Maximum Marks : 70*

---

*Note : Attempt any five questions. All questions carry equal marks.*

---

1. (a) Explain the difference between : 6
- (i) Potential and potential difference
  - (ii) Resistance and resistivity
  - (iii) Active and passive element
- (b) State and explain Ohms Law. What are the limitations of Ohm's Law ? 4
- (c) An Electric iron is rated as 1kW, 250V. Calculate the current taken by it if it is connected to 220V, 50Hz ac supply. 4
2. (a) Two resistances connected in series having  $18\Omega$  equivalent resistance and when connected in parallel having  $4\Omega$  equivalent resistance. Find the value of each resistance. 7

- (b) Calculate equivalent resistance between a-b terminal of the network, shown in fig - 1. 7

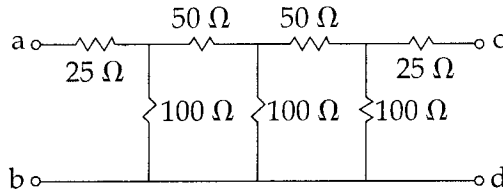


Fig. 1

3. (a) Find current flowing in each branch of the network as shown in fig. 2 using Nodal analysis. 7

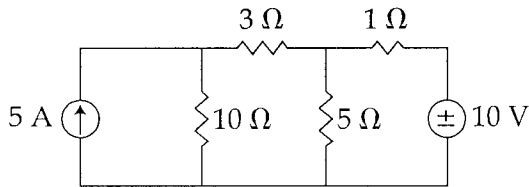


Fig. 2

- (b) Find equivalent resistance across a-b terminal of the network shown in fig. 3. 7

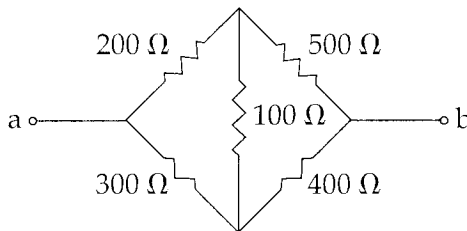


Fig. 3

4. (a) State and prove maximum power transfer theorem. 7  
 (b) State and explain Thevenin Theorem. List the steps required to obtain the Thevenin's equivalent circuit. 7
5. Find rms and average value of half wave rectifier output wave form as shown in fig. 4. 14

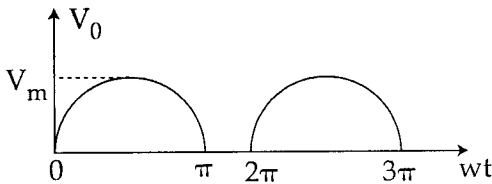


Fig. 4

6. (a) A voltage of  $200 \sin 100\pi t$  is applied to a coil having  $R = 200 \Omega$  and  $L = 0.38 \text{ H}$ . Find the expression for current and power taken by coil. 7  
 (b) Explain the following terms as applied to ac circuits. 7  
 (i) Impedance  
 (ii) Power factor  
 (iii) Phase angle
7. (a) Explain active power, reactive power and apparrant power. Also explain their significance. 7  
 (b) Explain resonance in parallel RLC circuit. Derive expression for resonance frequency. 7

8. Write short notes on **any four** of the following :

(a) Duality and dual network

**3.5x4=14**

(b) RLC series resonance

(c) Super position Theorem

(d) Star - delta Transformation

(e) Source Transformation

(f) Norton Theorem

---