

**B.Tech. Civil (Construction Management)/
B.Tech. Civil (Water Resources Engineering)**

01465

**Term-End Examination
June, 2014**

**ET-202(B) : PRINCIPLES OF ELECTRICAL
SCIENCES**

Time : 3 hours

Maximum Marks : 70

*Note : Answer any **five** questions. Symbols and abbreviations have their usual meaning. Use of calculator is permitted.*

1. (a) State and explain Thevenin's theorem with suitable example. 7
- (b) Explain the (i) star to delta and (ii) delta to star conversion. 7
2. (a) What is the function of a neutral wire in a 3-phase 4-wire system ? What current does it carry in a balance system ? 6
- (b) A system has $H(s) = 1/(s + 2)$. Negative feedback is employed with a feedback factor. Find the system function with feedback and also write the advantage of negative feedback. 8

3. (a) What are the different torques required in an indicating type instrument ? Draw and explain the working of attraction type moving iron instrument. 8
- (b) Write short notes on any *two* : 3×2=6
- (i) PMMC instrument.
 - (ii) Accuracy and resolution of an instrument.
 - (iii) Rectifier instrument.
4. (a) An electric motor is given an electric supply of 100 kW. It drives a mechanical load of constant torque at a speed of 1000 rpm. If the electromagnetic losses are 3.5 kW and the mechanical losses are 1.8 kW, find : 8
- (i) The mechanical power output
 - (ii) Output torque
 - (iii) Efficiency
- (b) Write short notes on any *two* : 3×2=6
- (i) Open and short circuit test in a single phase transformer.
 - (ii) Efficiency and losses in transformer.
 - (iii) Equivalent circuit refers to primary or secondary.
5. (a) Draw the V – I characteristics of a diode. An ideal diode is in series with a 1 kV resistor. A 5 V battery is applied to the network so as to forward bias the diode. Determine current through the diode. 6
- (b) Explain the transistor as controlled switch and as an amplifier. 8

6. (a) Draw and explain the Wein bridge oscillator. Design a Wein bridge oscillator for a frequency of 1 kHz. 7
- (b) Differentiate between astable and monostable multivibrator and explain them in brief. 7
7. (a) Explain following instructions in a microprocessor : 6
- (i) XTHL
 - (ii) RIM
 - (iii) DAD B
 - (iv) RRC
- (b) Explain : 8
- (i) Interrupts
 - (ii) Serial I/O
 - (iii) Direct Memory Access
8. (a) Convert R-S Flip-flop into D Flip-flop and explain. 7
- (b) Implement XOR Gate using Universal Gate. 7