

**B.Tech. ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

00884

**Term-End Examination**

**June, 2014**

**BIEL-011 : LINEAR INTEGRATED CIRCUITS**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any **seven** questions. Assume suitable data, wherever required. Use of scientific calculator is permitted.*

---

1. Define input offset voltage and CMRR as applied to OP-AMP IC's. Explain how the above parameters can be measured. 10
  
2. Draw the schematic of a low pass active filter and explain the operation. Also plot the gain/frequency response. 10
  
3. (a) Draw and explain the functional block diagram of an OP-AMP. 6  
(b) Discuss briefly the power supply requirements of an OP-AMP. 4
  
4. (a) What is the purpose of compensating networks in OP-AMPs ? What is meant by compensated and non-compensated OP-AMP ? 7  
(b) Write the applications of a sawtooth generator. 3

5. (a) Draw a cascade differential amplifier circuit, and explain briefly. 5
- (b) With the help of circuit diagram, explain current mirror circuit. 5
6. Draw and explain a Wein bridge oscillator with adaptive negative feedback. 10
7. Explain the circuit of a zero crossing detector. Also draw its input and output waveforms. 10
8. (a) Explain the working of switched mode power supplies. 5
- (b) Design a compensatory network for an OP-AMP using  $\pm 15$  V supply voltages with  $V_{i0} = 10$  mV (maximum), and  $R_c = 10 \Omega$ . 5
9. (a) Draw the circuit diagram of an OP-AMP used as an inverting amplifier with negative feedback and derive the expression for its gain. 7
- (b) What is the role served by clipper circuit? 3
10. Write short notes on any *two* of the following:  $2 \times 5 = 10$
- (a) Sample and hold circuit
- (b) Voltage to current convertors
- (c) Current mirror and level translator