

**B.Tech. - VIEP - ELECTRICAL ENGINEERING  
(BTELVI)**

00006

**Term-End Examination**

**June, 2014**

**BIEE-014 : NETWORK THEORY**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any seven questions. All questions carry equal marks.*

---

---

1. (a) Find the Cauer-I form of RC network.

$$z(s) = \frac{(s + 3)(s + 6)}{(s + 1)(s + 5)}$$

- (b) State and prove the maximum power transfer theorem with suitable example and state the maximum efficiency.  $5 \times 2 = 10$

2. (a) Describe the relationship between twigs and links and also write the properties of a tree in a network.

- (b) Determine the voltage ratio transfer function  $V_o(s) / V_i(s)$  for a ladder network shown in Fig. 1.

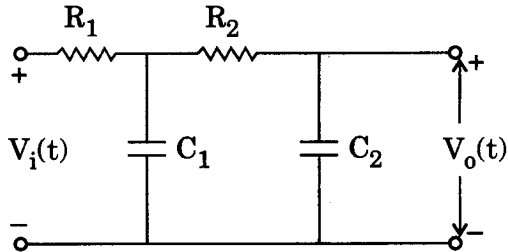


Fig. 1

5×2=10

3. (a) Describe the graphical method to determine the frequency response from the pole-zero plot.

- (b) Given a simple circuit of a K-type band pass filter; show that its resonance frequency is the geometric mean of the cut-off frequencies.

5×2=10

4. (a) Establish the conditions of (i) symmetry, (ii) reciprocity in terms of ABCD parameters of a linear, passive two-port network.

- (b) Find the z-parameters of the two-port network shown in Fig. 2. Hence prove that the y-parameters of this network do not exist.

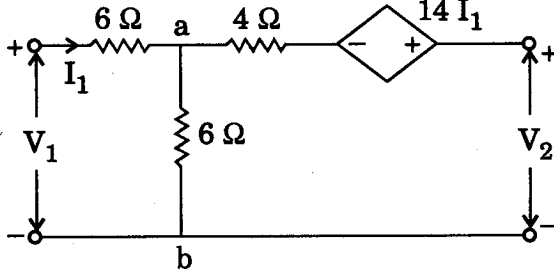


Fig. 2

5×2=10

5. State and prove the Superposition theorem with the help of suitable examples and also write its limitations. 10
6. State and explain the Millman's theorem and also find the current in load  $Z_L$  shown in Fig. 3. 10

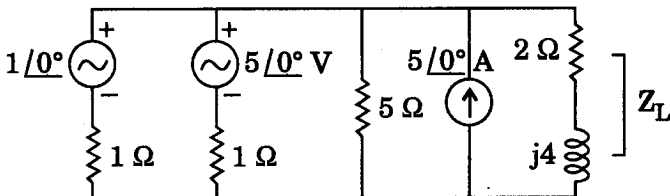


Fig. 3

7. Draw the oriented graph of the network shown in Fig. 4 and write the incidence matrix by inspection. 4+6=10

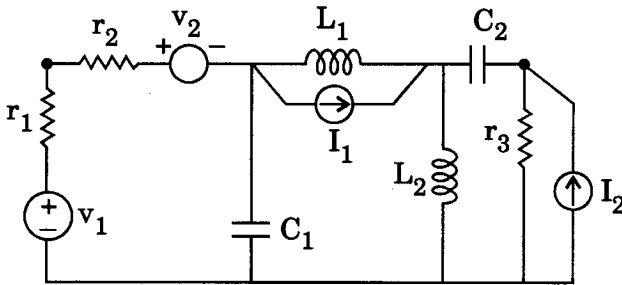


Fig. 4

8. Plot the pole and zeros of  $H(s) = \frac{4s}{s^2 + 2s + 2}$  and use it to plot magnitude and phase characteristics for  $\omega = 0, 1, 1.5, 3$  and  $5$ . 10
9. Design a band pass constant K filter with cut-off frequency of 3 kHz and 6 kHz and nominal characteristics impedance of 600  $\Omega$ . 10
10. Explain with illustrative examples the meaning of the following terms : 10
- (i) Incidence matrix
  - (ii) Cut-set matrix
  - (iii) Fundamental loop matrix