

**DIPLOMA - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(DECVI)/ADVANCED LEVEL CERTIFICATE  
COURSE IN ELECTRONICS AND  
COMMUNICATION ENGINEERING (ACECVI)**

**Term-End Examination**

**June, 2014**

**BIEL-028 : CIRCUITS AND NETWORKS**

*Time : 2 hours*

*Maximum Marks : 70*

---

*Note : Attempt five questions. Question no. 1 is compulsory. Use of scientific calculator is permitted.*

---

---

1. Select the correct answer :  $7 \times 2 = 14$
- (a) One sine wave has a period of 2 ms, another has a period of 5 ms, and another has a period of 10 ms. Which sine wave is changing at a faster rate ?
- (i) sine wave with period 2 ms
  - (ii) sine wave with period 5 ms
  - (iii) sine wave with period 10 ms
  - (iv) All are at the same rate

(b) What is the phase angle between the inductor current and the applied voltage in a parallel RL circuit ?

- (i)  $0^\circ$
- (ii)  $45^\circ$
- (iii)  $90^\circ$
- (iv)  $30^\circ$

(c) The superposition theorem is valid


- (i) only for a.c. circuits
- (ii) only for d.c. circuits
- (iii) for both a.c. and d.c. circuits
- (iv) None of the above

(d) What is the total reactance of a series RLC circuit at resonance ?


- (i) Equal to  $X_L$
- (ii) Equal to  $X_C$
- (iii) Equal to R
- (iv) Zero

- (e) The resultant voltage in a closed balanced delta circuit is given by
- (i) three times the phase voltage
  - (ii)  $\sqrt{3}$  times the phase voltage
  - (iii) zero
  - (iv)  $\frac{1}{3}$  times the phase voltage
- (f) Transient behaviour occurs in any circuit when
- (i) there are sudden changes of voltage
  - (ii) the voltage source is shorted
  - (iii) the circuit is connected or disconnected from the supply
  - (iv) All of the above happen
- (g) The Laplace transform of the first derivative of a function  $f(t)$  is
- (i)  $\frac{F(s)}{s}$
  - (ii)  $sF(s) - f(0)$
  - (iii)  $F(s) - f(0)$
  - (iv)  $f(0)$

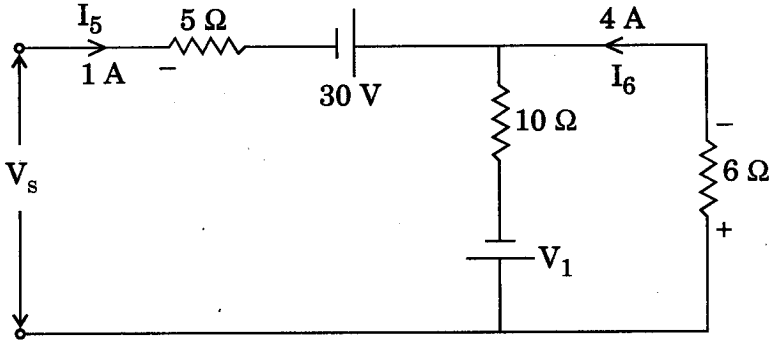
2. (a) Find the current in the  $10\ \Omega$  resistance. Also calculate the value of  $V_1$  and  $V_s$  in the circuit.



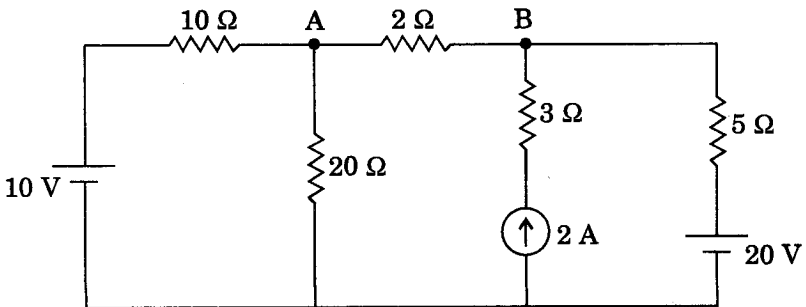- (b) Find the voltage across the  $2\ \Omega$  resistor, by using the superposition theorem.  $2 \times 7 = 14$



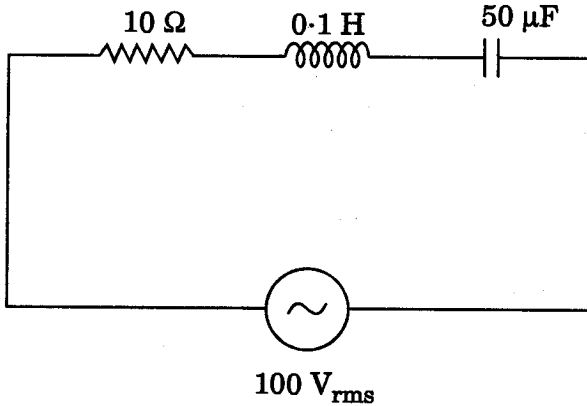
3. (a) For the circuit shown, determine the frequency at which the circuit resonates. Also find the voltage across the inductor at resonance and the Q factor of the circuit.




- (b) Obtain the expression for the frequency at which the maximum voltage occurs across the capacitor in series resonance circuit in terms of Q factor and resonance frequency.

$2 \times 7 = 14$

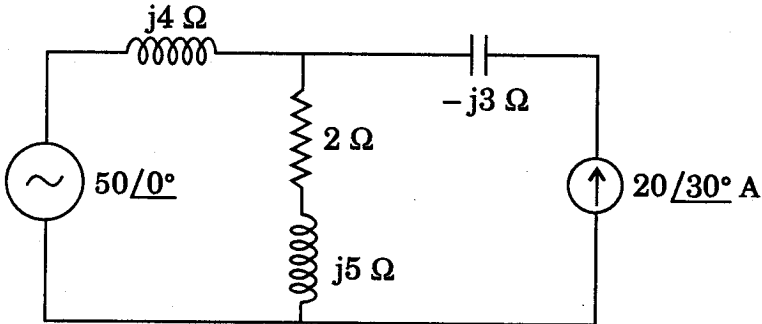
4. (a) Determine the voltage across  $(2 + j5) \Omega$  impedance as shown in fig. by using superposition theorem.



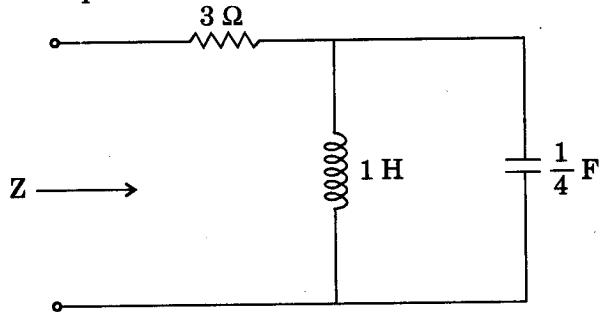- (b) Transform the circuit shown in fig. to the s-domain and determine the Laplace impedance  $Z(s)$ .  $2 \times 7 = 14$



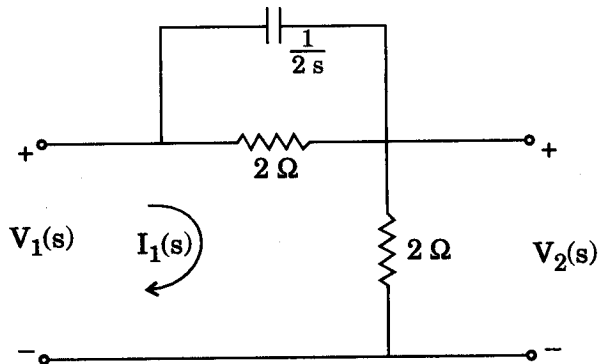5. (a) Design a low pass filter (T-sections) having a cut-off frequency of  $2 \text{ kHz}$  to operate with a terminated load resistance of  $500 \Omega$ .
- (b) Design a  $\pi$ -type attenuator to give  $20 \text{ dB}$  attenuation and to have a characteristic impedance of  $100 \Omega$ .  $2 \times 7 = 14$
6. (a) Explain the necessary conditions for the transfer functions.
- (b) For the network shown in fig. obtain the transfer functions  $G_{21}(s)$ ,  $Z_{21}(s)$  and driving point impedance  $Z_{11}(s)$ .  $2 \times 7 = 14$



7. (a) Express Z-parameters in terms of Y-parameters.
- (b) Derive the condition for symmetry in terms of Y (admittance) parameters.  $2 \times 7 = 14$

8. Write short notes on any *two* parts from each section (a) and (b) :

- (a) (i) Image impedance  
(ii) Transient state  
(iii) Phasor notations  $2 \times 3 \frac{1}{2} = 7$

- (b) (i) Cascade connection in Two-port network  
(ii) Ladder network  
(iii) Gate function  $2 \times 3 \frac{1}{2} = 7$
-