

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)**

00495

Term-End Examination

June, 2014

BIELE-005 : INDUSTRIAL ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : Attempt any **five** questions including Question no. 1 which is compulsory. All questions carry equal marks. Missing data may be assumed suitably.

1. Attempt all objective type questions : 7×2=14
- (a) In a diode, the cut-in voltage and forward voltage drop are respectively.
- (i) 0.7 V, 0.7 V
- (ii) 0.7 V, 1 V
- (iii) 0.7 V, 0.6 V
- (iv) 1 V, 0.7 V
- (b) As compared to Power MOSFET, a BJT has
- (i) lower switching losses but higher conduction loss
- (ii) higher switching losses and higher conduction loss

- (iii) higher switching losses but lower conduction loss
 - (iv) lower switching losses and lower conduction loss
- (c) In a thyristor, anode current is made up of
- (i) electrons only
 - (ii) electrons or holes
 - (iii) electrons and holes
 - (iv) holes only
- (d) In a thyristor, ratio of latching current to holding current is
- (i) 0.4
 - (ii) 1.0
 - (iii) 2.5
 - (iv) 6.0
- (e) In a UJT, with V_{BB} as voltage across two base terminals, the emitter potential at peak point is given by
- (i) ηV_{BB}
 - (ii) ηV_D
 - (iii) $\eta V_{BB} + V_D$
 - (iv) $\eta V_D + V_{BB}$

- (f) In a single-phase semi-converter, for continuous conduction, freewheeling diode conducts for
- (i) α
 - (ii) $\pi - \alpha$
 - (iii) π
 - (iv) $\pi + \alpha$
- (g) In a 1 - ϕ full converter, if load current is I and ripple free, then average thyristor current is
- (i) $\frac{1}{2} I$
 - (ii) $\frac{1}{3} I$
 - (iii) $\frac{1}{4} I$
 - (iv) I
2. (a) Explain steady-state characteristics for BJTs.
- (b) Explain BJT switching performance. $7+7=14$
3. (a) Explain static $V - I$ characteristics of a thyristor.
- (b) Explain forward voltage triggering and gate triggering turn-on methods for a thyristor. $7+7=14$
4. (a) Write short notes on the following :
- (i) TRIAC
 - (ii) SUS

- (b) A Relaxation Oscillator using a UJT, as shown in Figure 1 is to be designed for triggering an SCR. The UJT has the following characteristics :

$\eta = 0.72$, $I_P = 0.6 \text{ mA}$, $V_P = 18.0 \text{ V}$,
 $V_V = 1.0 \text{ V}$, $I_V = 2.5 \text{ mA}$, $R_{BB} = 5 \text{ k}\Omega$,
 normal leakage current with emitter open = 4.2 mA .

The firing frequency is 2 kHz . For $C = 0.04 \text{ }\mu\text{F}$, compute the value of R , R_1 and R_2 .

7+7=14

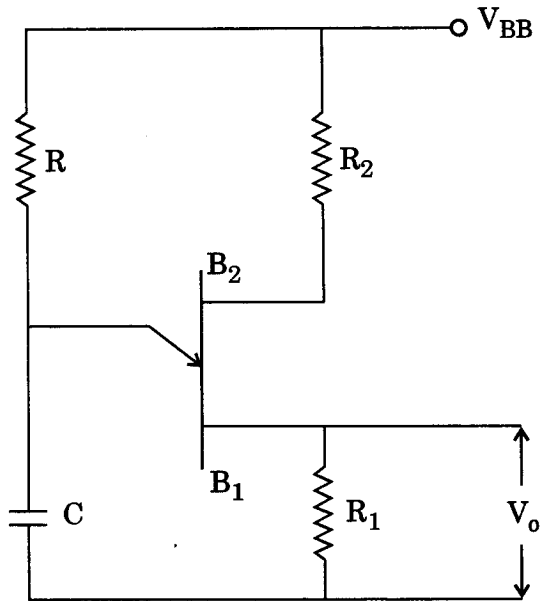


Figure 1

5. (a) A $1 - \phi$ half wave SCR circuit feeds power to a resistive load. Draw waveforms for load current and voltage across the SCR for a given firing angle α .
- (b) A resistive load of 10Ω is connected through a half wave SCR circuit to 220 V, 50 Hz, $1 - \phi$ source. Calculate the power delivered to load for a firing angle of 60° . Find also the value of input power factor. $7+7=14$
6. (a) For a $1 - \phi$ one pulse controlled converter system, sketch waveforms for load voltage and load current for (i) RL load and (ii) RL load with freewheeling diode across RL.
- (b) A 230 V, 50 Hz, one pulse SCR controlled converter is triggered at firing angle of 40° and load current extinguishes at an angle of 210° . Find average output voltage and average load current for $R = 5 \Omega$ and $L = 2 \text{ mH}$. $7+7=14$

7. (a) Explain working of 3 - ϕ full controlled rectifier.

(b) A 3 - ϕ full converter charges a battery from a 3 - ϕ supply of 230 V, 50 Hz. The battery emf is 200 V and its internal resistance is 0.5 Ω . On account of an inductance connected in series with battery whose charging current is constant at 20 A, compute firing angle delay and the supply power factor.

7+7=14
