

**DIPLOMA - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(DECVI)**

00405

**Term-End Examination**

**June, 2014**

**BIELE-006 : ELECTRONIC PRODUCT DESIGN**

*Time : 2 hours*

*Maximum Marks : 70*

---

**Note :** Attempt any **five** questions. Each question carries equal marks.

---

---

1. (a) Explain input Power consideration and Protection circuit for MCB. 7  
(b) What do you mean by over-voltage ? Explain the indicators for the over-voltage. 7
  
2. Describe design steps for Vending Machine using ASM technique. Explain the implementation of the design. 14
  
3. (a) What do you mean by sequence generator ? Also explain its working. 7  
(b) Implement 2 : 4 decoder using NOR gates only. 7

4. Explain the steps in designing using PAL. Also draw the PAL equivalent for the following Boolean equation : 14

$$X = a'b + a'bc$$

$$Y = c' + ab$$

5. (a) Find out the transfer function of a second order band pass filter. 7

- (b) Describe the KRC filter and derive its transfer function. 7

6. (a) What do you mean by cascading of a filter ? 7

- (b) How is ROM classified ? Explain each of the classifications. 7

7. How a LED is interface with a micro-controller ? Give your answer with suitable programming steps. 14

8. (a) Draw the interfacing diagram of an analog to digital convertor using micro-controller. 7

- (b) Differentiate between combinational and sequential logic circuits. 7

---