

**DIPLOMA IN ELECTRICAL ENGINEERING  
(DELVI)**

00521


**Term-End Examination****June, 2014****BIEE-033 : ELECTRICAL CIRCUIT THEORY***Time : 2 hours**Maximum Marks : 70*

---

**Note :** *Attempt any five questions. All questions carry equal marks.*

---

1. (a) Explain the difference between 6
- (i) dc voltage and ac voltage
  - (ii) Thevenin's equivalent and Norton's equivalent
  - (iii) Unilateral and Bilateral element
- (b) State and explain Ohm's law. What are the limitation of Ohm's Law ? 4
- (c) Determine the resistance between the terminals a-b in the network shown in Fig. 1. 4

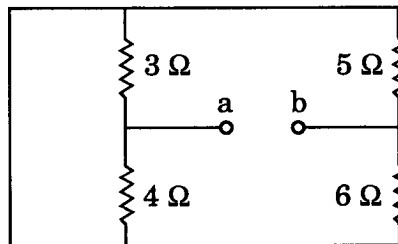*Fig. 1*

2. (a) Find the input resistance at AB for the lattice network shown in Fig. 2 when terminals CD are
- open circuited.
  - short circuited.

7

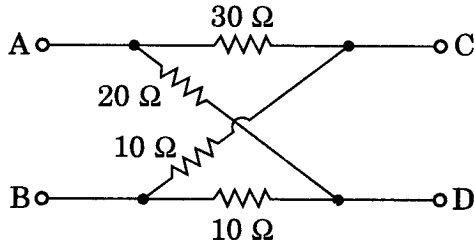


Fig. 2

- (b) Convert the  $\Pi$ -network to its T-equivalent as shown in Fig. 3.

7

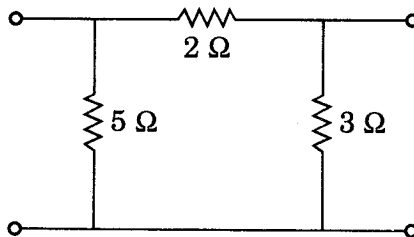


Fig. 3

3. (a) State and prove the maximum power transfer theorem.
- (b) State Superposition theorem and explain it with a suitable example.
4. (a) Which method is more suitable to solve a particular circuit, Mesh analysis or Nodal Analysis and why?

7

7

4

- (b) Determine the current through  $5\ \Omega$  resistor in Fig. 4 using both Thevenin's and Norton's Theorem. 10

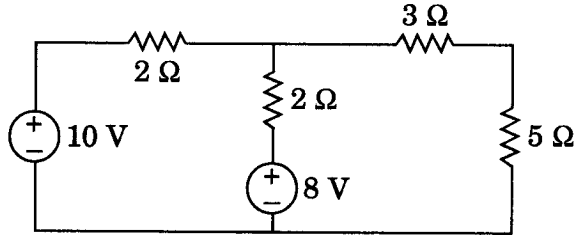


Fig. 4

5. Find rms and average value of half wave rectifier wave output. Also find out rectification efficiency and ripple factor for the above case. 14
6. (a) A series RLC circuit has  $R = 10\ \Omega$ ,  $L = 0.1\ \text{H}$  and  $C = 8\ \mu\text{F}$ . Determine
- (i) the resonant frequency
  - (ii) Q-factor of the circuit at resonance
  - (iii) the half-power frequency 7
- (b) Draw the tank circuit and determine the expression of dynamic impedance  $Z_0$  and resonant frequency  $\omega_0$ . 7
7. (a) Find equivalent resistance across a - b terminal of network shown in Fig. 5. 7

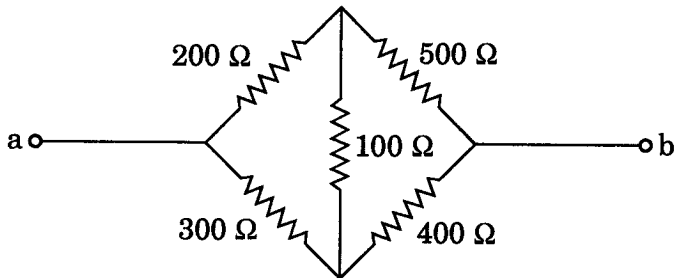


Fig. 5

- (b) In the network shown in Fig. 6, determine

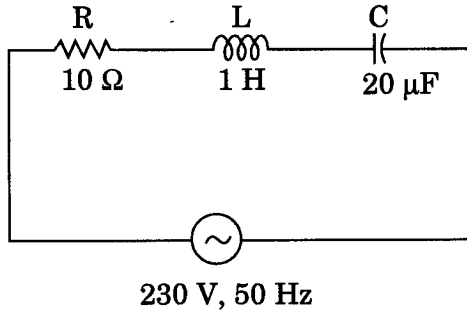


Fig. 6

- (i) total impedance
  - (ii) total current
  - (iii) current in each branch
  - (iv) overall power factor
  - (v) volt-ampere
  - (vi) active power
  - (vii) reactive volt-ampere 7
8. Write short notes on any **four** of the following :  $4 \times 3 \frac{1}{2} = 14$
- (a) Reactive power in purely inductive circuit
  - (b) Power factor improvement
  - (c) Star-Delta Transformation
  - (d) Voltage Magnification
  - (e) Variation of  $Z$ ,  $X_L$ ,  $X_C$ ,  $R$ ,  $\cos \phi$ ,  $I$  with respect to  $f$