

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

00166

**Term-End Examination
June, 2016**

BIEL-005 : ANALOG ELECTRONIC CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. All questions carry equal marks. Any missing data may be suitably assumed and mentioned. Use of scientific calculators is permitted.

1. For the network shown in Figure 1, determine $4 \times 2 \frac{1}{2} = 10$

- (a) r_e
- (b) Z_i
- (c) Z_o
- (d) A_v

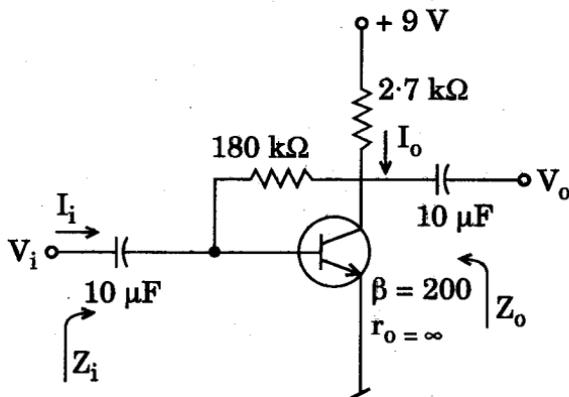


Figure 1

2. Calculate the following for the Darlington emitter-follower circuit shown in Figure 2. $4 \times 2 \frac{1}{2} = 10$

- Input Impedance (Z_i) if $r_i = 5 \text{ k}\Omega$
- AC Current Gain (A_i)
- Output Impedance (Z_o)
- AC Voltage Gain (A_v)

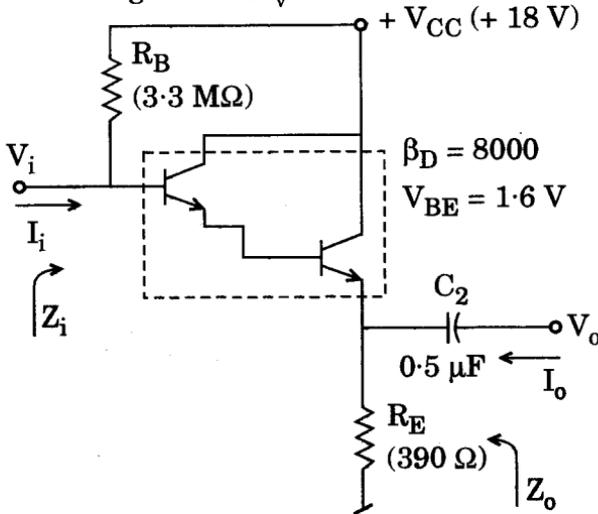


Figure 2

3. (a) Explain Multi-stage Frequency Effects. Assuming 'n' identical stages of amplifiers cascaded together, show that for the low-frequency region and the high-frequency region, the cut-off frequency of the multi-stage amplifier is given respectively by the expressions given below :

- Low-frequency region

$$f'_1 = \frac{f_1}{\sqrt{2^{1/n} - 1}}$$

- High-frequency region

$$f'_2 = f_2 \left(\sqrt{2^{1/n} - 1} \right)$$

- (b) A two-stage amplifier has a first stage gain of 50 dB and a second stage gain of 20 dB. What is the overall gain of the amplifier in dB ? 7+3=10
4. (a) Explain the operation of a Class-B push-pull amplifier with the help of a neatly labelled block diagram.
- (b) Prove that the maximum efficiency of a Class-B amplifier is 78.5%. 5+5=10
5. What are the advantages and disadvantages of tuned amplifiers ? With the help of a neatly labelled diagram, explain the operation of a single tuned amplifier giving its frequency response curve. 10
6. Explain the effect of negative feedback on the following : 5×2=10
- (a) Input Impedance
- (b) Output Impedance
- (c) Gain
- (d) Noise
- (e) Frequency Response
7. Give the circuit diagram of a crystal-controlled oscillator using a crystal in series-feedback path. Derive an expression for its input impedance and the frequency of oscillation. 3+7=10
8. Give the internal block diagram of IC-555 timer and enlist the functions performed by each pin. 10

9. Explain the operation of an astable and a monostable multivibrator using IC-555 with the help of a neatly labelled circuit diagram. $5+5=10$

10. Write short notes on any *two* of the following : $2 \times 5 = 10$

- (a) Wein-Bridge Oscillator
 - (b) Double Tuned Amplifiers
 - (c) High-frequency Model for CE Configuration
-