

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

June, 2016

00636

**BIEL-012 : ANALOG AND MIXED MODE VLSI
DESIGN**

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. All questions carry equal marks. Missing data, if any, may be suitably assumed. Use of scientific calculator is permitted.

1. (a) What are the typical characteristics of a sample-and-hold (S/H) circuit ? Explain in brief. 5

- (b) Explain the need for converting an analog signal to a digital-discrete signal. 5

2. With the help of a neatly labelled block diagram, explain the following : 5+5=10
 - (a) Pipeline DAC
 - (b) Pipeline ADC

3. Explain the procedure involved in improving Signal-to-Noise Ratio (SNR) using averaging techniques in data converter circuits. 10
4. What is the need of decimating filters in ADC circuits ? How can they improve its performance ? Explain. 10
5. List out the specifications of DAC and ADC. Find the resolution of a DAC, if the output voltage is desired to change in 1 mV increments using a reference voltage of 5 V. 10
6. Derive an expression for transconductance (g_m) and output resistance (r_o) for a MOSFET operating in triode region. Also establish a relationship between the two parameters of the MOSFET. 3+3+4=10
7. With the help of a neatly labelled block diagram, explain the operation of a 2-step Flash analog-to-digital converter circuit (ADC). 10
8. What are the various design issues associated with the scaling procedure in sub-micron CMOS technology ? Explain them briefly. 10
9. What are Bidirectional switches ? Explain with the help of a neatly labelled circuit, how MOSFETs can be used as a bidirectional switch. 3+7=10

10. Write short notes on any *two* of the following: *2×5=10*

- (a) Level Shifting
 - (b) Interpolating Filters for DAC
 - (c) Analog Multiplier
-