

**B.Tech. - VIEP - ELECTRICAL ENGINEERING
(BTELVI)****Term-End Examination****June, 2016**

00226

BIEE-024 : POWER ELECTRONICS*Time : 3 hours**Maximum Marks : 70*

Note : Attempt any **seven** questions. All questions carry equal marks. Missing data may be suitably assumed. Use of scientific calculator is permitted.

1. (a) Explain the I – V characteristics of SCR. 5
- (b) What is the difference between a thyristor and a TRIAC ? Draw and explain the V – I characteristics of TRIAC. 5
2. (a) What is reverse recovery time of the power semiconductor diode ? The forward voltage drop of a power diode is $V_D = 1.2$ V at $I_D = 300$ A. Assuming that $n = 2$ and $V_T = 25.7$ mV, find the reverse saturation current (I_S). 5
- (b) What is the purpose of dv/dt protection ? What is the common method of dv/dt protection ? 5

3. (a) Differentiate between semi-converter and full converter circuit. Draw any one semi-converter and full-converter circuit. 5
- (b) Explain gate trigger controller circuit of SCR. 5
4. Draw the two-transistor model of a thyristor. Explain the turn-off and turn-on characteristics of a thyristor. 5+5
5. Ten thyristors are used in a string to withstand a d.c. voltage of $V_s = 15 \text{ kV}$. The maximum leakage current and recovery charge differences of the thyristors are 10 mA and $150 \mu\text{C}$, respectively. Each thyristor has a voltage-sharing resistance of $R = 56 \text{ k}\Omega$ and capacitance of $C_1 = 0.5 \mu\text{F}$. Determine
- (a) the maximum steady state voltage sharing $V_{DS(\text{max})}$,
- (b) the steady state voltage derating factor,
- (c) the maximum transient voltage sharing $V_{DT(\text{max})}$, and
- (d) the transient voltage derating factor. 10
6. Draw and explain the working of a single-phase dual converter. Also draw its $V-I$ characteristics. What is the cause of circulating current in dual converters? 5+3+2

7. What are the main effects of source inductance for a full-converter? A three-phase full-converter is fed by 400 volts, three-phase, 50 Hz supply. The average load current is 150 A and the load is highly inductive. For a firing angle of 60° , find the output power, average output voltage, rms and peak current through the thyristors and peak inverse voltage. 3+7

8. With the help of a neat circuit diagram and waveforms, explain briefly the operation of a transistorised 3-phase bridge inverter with resistive load in 180° conduction mode. 10

9. Circuit in Figure 1 employing complementary commutation has $V_s = 200$ V, $R_1 = 10 \Omega$ and $R_2 = 100 \Omega$. Determine the

- (a) peak value of current through thyristors T_1 and T_2 ,
- (b) value of capacitor C if each thyristor has a turn-off time of $40 \mu\text{s}$. Take a factor of safety 2. 10

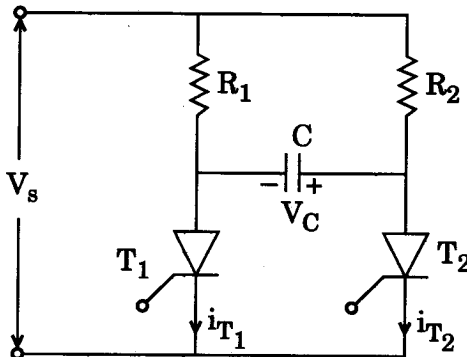


Figure 1

10. Write short notes on any *two* of the following : $2 \times 5 = 10$

- (a) Thyristor Firing Circuits
 - (b) Series and Parallel Connections of Diode
 - (c) Impulse Commutation
 - (d) Sinusoidal Pulse Width Modulation (SPWM)
-