

**B.Tech. – VIEP – ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

**June, 2017**

00504

**BIEL-003 : DIGITAL ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any **seven** questions. All questions carry equal marks. Assume any missing data suitably. Use of scientific calculator is allowed.*

---

---

1. (a) Perform  $(54)_{10} - (27)_{10}$  using 2's complement. 5
- (b) Convert the following expressions into their canonical forms : 5
  - (i)  $F = AB + ACD + \bar{A}BC$
  - (ii)  $F = (A + B)(A + \bar{C})(B)$
2. (a) Design and implement a 3-bit magnitude comparator. 5
- (b) Design a 4-bit parallel adder. 5

3. (a) What do you mean by Master-Slave flip-flop ? How does it avoid the race around condition ? 5
- (b) What do you mean by characteristic equation of flip-flop ? Derive it for JK flip-flop. 5
4. (a) Differentiate between asynchronous and synchronous counter. 5
- (b) Design a 3-bit bidirectional synchronous counter using T-flip-flop. 5
5. What do you mean by tri-state logic ? Draw and explain the working of a tri-state TTL NAND gate. 3+7=10
6. (a) Design and implement  $64k \times 8$  RAM using  $8k \times 8$  RAM. 5
- (b) Explain how a CMOS logic IC can be driven by a TTL logic IC. 5
7. (a) Draw and explain the working of a 4-bit SISO shift register with appropriate timing waveform. 5
- (b) Explain the concept and design procedure of Algorithmic State Machines (ASM). 5

8. Simplify the given Boolean expression using K-map :

$$F = \sum m(0, 1, 3, 7, 11, 15) + d(2, 4, 6)$$

Also implement the simplified expression using NOR gate. 10

9. (a) For a 2-bit number  $x$ , design and implement  $y = 5x^2 + 6x + 1$  using PLA. 5
- (b) What do you mean by semiconductor memories? How do you classify them? 5
10. (a) Obtain Excess-3 and Gray code for the following : 5
- (i)  $(1453)_{10}$
- (ii)  $(56)_{10}$
- (b) Design and implement a 4-bit binary adder and subtractor. 5
-