

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

00294

June, 2017

BIEL-011 : LINEAR INTEGRATED CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : *Attempt any seven questions. Missing data, if any, may be suitably assumed. Use of scientific calculator is permitted.*

1. What is a current mirror ? Discuss in detail about the Wilson current source. 10
2. Find the slew rate of a frequency compensated op-amp at room temperature which has a unity crossover frequency of 5 MHz. 10
3. Define CMRR, SVRR, input offset current. Also state the reasons for the offset currents at the input of the op-amp. 10

4. Draw the high frequency equivalent circuit of an op-amp. Derive an expression for the open-loop voltage gain as a function of frequency. 10
5. Draw the circuit of an Astable multivibrator using op-amp and derive an expression for its frequency of oscillation. 10
6. What are the advantages of switch mode power supplies ? Also list the important parts of regulated power supply. 10
7. (a) With neat schematic representations, explain the operation of Active Positive Clamper to clamp the input signal above ground state by 5 V. 6
- (b) State the applications of Sample and Hold circuits. 4
8. (a) Explain the basic comparator and its characteristics. 4
- (b) Design an amplifier with a gain of -10 and input resistance of 10 K . 6
9. (a) Draw an adder circuit using op-amp to get the output expression as

$$V_o = -(0.1V_1 + V_2 + 5V_3).$$
 6
- (b) List the applications of Log amplifiers. 4

10. Write short notes on any **two** of the following : 2×5=10

- (a) Current-to-Voltage Converters
 - (b) Frequency Response of Compensated Op-amp
 - (c) Wein Bridge Oscillator
-

