

**DECVI / DELVI / DCSVI / ACECVI / ACELVI /
ACSVI**

Term-End Examination

June, 2017

00294

BIEL-027 : APPLIED ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : *Attempt any **five** questions. Question number 1 is **compulsory**. Use of scientific calculator is permitted. Symbols have their usual meaning.*

1. (a) The action of a JFET in its equivalent circuit can be best represented as a
 - (i) Current Controlled Voltage Source (CCVS)
 - (ii) Current Controlled Current Source (CCCS)
 - (iii) Voltage Controlled Voltage Source (VCVS)
 - (iv) Voltage Controlled Current Source (VCCS)

- (b) Negative feedback in an amplifier
- (i) improves SNR at the input
 - (ii) improves SNR at the output
 - (iii) does not affect the SNR at the output
 - (iv) reduces distortion
- (c) Crossover distortion behaviour is a characteristic of
- (i) Class A output stage
 - (ii) Class AB output stage
 - (iii) Class B output stage
 - (iv) Common base output stage
- (d) The MOSFET switch in its ON-state may be considered to be equivalent to the
- (i) Resistor
 - (ii) Inductor
 - (iii) Capacitor
 - (iv) Battery
- (e) Oscillation frequency in Hartley oscillator is
- (i) $f = \frac{1}{2\pi\sqrt{LC}}$
 - (ii) $f = \frac{1}{2\pi\sqrt{(L_1 + L_2 + 2m) \cdot C}}$
 - (iii) $f = \frac{1}{2\pi\sqrt{RC}}$
 - (iv) $f = \frac{1}{2\pi\sqrt{(L_1 + L_2) - C}}$

(f) A bootstrap sweep circuit employs _____ type of feedback.

- (i) positive
- (ii) negative
- (iii) multiply
- (iv) divide

(g) UJT is also known as

- (i) positive resistance device
- (ii) negative temperature device
- (iii) negative resistance device
- (iv) positive temperature device

7×2=14

2. (a) Write down the advantages, disadvantages and applications of class A and class AB power amplifiers. 7

(b) If a JFET has $I_{DSS} = 12 \text{ mA}$, $V_P = -4 \text{ V}$, calculate the operating point (I_{DS} , V_{DS}) of the JFET in the circuit of Figure 1. 7

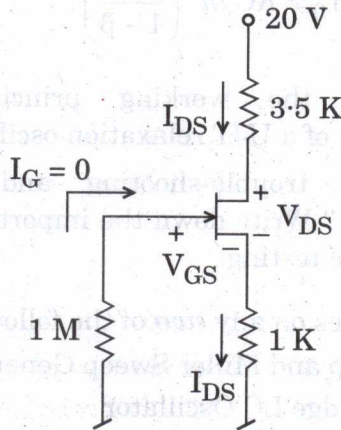


Figure 1

3. (a) Why is a tuned amplifier required in analog circuits ? Explain the operating principle of a single tuned amplifier with necessary diagrams. 7
- (b) An RC phase shift oscillator generates sinusoidal output of 10 kHz. If a BJT has $h_{fe} = 60$, $h_{ie} = 2 \text{ k}\Omega$ and $R_C = 5 \text{ k}\Omega$, calculate the values of R and C used in the feedback network. 7
4. (a) What are the necessary conditions of oscillations ? Compare negative and positive feedback systems. 7
- (b) Draw the circuit diagram of an RC integrator and explain its operation with required waveforms. 7
5. Draw and explain the operation of a monostable multivibrator with necessary diagram and waveforms. Also derive the expression for the pulse duration $T_0 \simeq RC \ln \left(\frac{1}{1 - \beta} \right)$. 7+7
6. (a) Describe the working principle and operation of a UJT relaxation oscillator. 7
- (b) Why is trouble-shooting and testing required ? Write down the important steps for visible testing. 7
7. Write short notes on any *two* of the following : $2 \times 7 = 14$
- (a) Bootstrap and Miller Sweep Generator
- (b) Wein Bridge LC Oscillator
- (c) Application of FET as VVR (Voltage Variable Resistor)