

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI) /
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination

June, 2017

00094

BIEL-030 : DIGITAL ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : Attempt any **five** questions. Question no. 1 is **compulsory**. Use of scientific calculator is allowed.

1. Choose the correct answer for the following : $7 \times 2 = 14$

(a) For the given logic circuit shown in Figure 1 below, the output Y is equal to

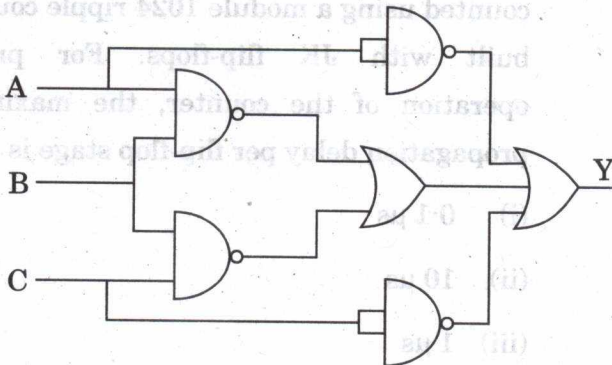


Figure 1

- (i) \overline{ABC}
- (ii) $\overline{A} + \overline{B} + \overline{C}$
- (iii) $\overline{AB} + \overline{BC} + \overline{A} + \overline{C}$
- (iv) $\overline{AB} + \overline{BC}$
- (b) 2's complement representation of a 16-bit number (one sign bit and 15 magnitude bits) is FFFF. Its magnitude in decimal representation is
- (i) 0
- (ii) 1
- (iii) 32·767
- (iv) 65·535
- (c) A pulse train with a frequency of 1 MHz is counted using a module 1024 ripple counter built with JK flip-flops. For proper operation of the counter, the maximum propagation delay per flip-flop stage is
- (i) 0·1 μ s
- (ii) 10 μ s
- (iii) 1 μ s
- (iv) 0·01 μ s

(d) The Boolean expression $\overline{A(B + \overline{C})D}$ is equal to

(i) $A + \overline{B} + \overline{C}D$

(ii) $\overline{A} + \overline{B} + C + D$

(iii) $\overline{A} + B + C + \overline{D}$

(iv) $\overline{A} + B + \overline{C} + \overline{D}$

(e) The speed of conversion is maximum in a

(i) Successive-approximation A/D converter

(ii) Parallel-comparative A/D converter

(iii) Counter ramp A/D converter

(iv) Dual slope A/D converter

(f) The gates required to build a Half adder are

(i) EX-OR gate and NOR gate

(ii) EX-OR gate and OR gate

(iii) EX-OR gate and AND gate

(iv) four NAND gates

(g) Which of the following is the fastest logic ?

(i) TTL

(ii) ECL

(iii) CMOS

(iv) LSI

2. (a) Minimize the logic function

$$Y(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14).$$

Use Karnaugh map. Draw the logic circuit for the simplified function. 10

- (b) Simplify the given expression to its Sum of Products (SOP) form. Draw the logic circuit for the simplified SOP function

$$Y = (A + B) (A + \overline{AB}) C + \overline{A} (B + \overline{C}) + \overline{A} B + ABC. \quad 4$$

3. (a) Design a 8-to-1 multiplexer by using the four-variable function given by

$$F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15). \quad 10$$

- (b) Convert the decimal number 82.67 to its binary, hexadecimal and octal equivalents. 4

4. (a) Prove the following Boolean identities : 6

(i) $XY + YZ + \overline{Y}Z = XY + Z$

(ii) $A \cdot B + \overline{A} \cdot B + \overline{A} \cdot \overline{B} = \overline{A} + B$

- (b) Add 648 and 487 in BCD code. 4

- (c) Add 20 and (-15) using 2's complement. 4

5. (a) Explain a half adder with the help of a truth table and logic diagram. 10
- (b) With the help of a suitable diagram, explain how to convert a JK flip-flop to a T-type flip-flop. 4
6. Using D flip-flops and waveforms, explain the working of a 4-bit SISO shift register. 14
7. (a) With the help of an R2R binary ladder, explain the working of a 4-bit D/A converter. 10
- (b) Compare the memory devices RAM and ROM. 4
-

...the ... of ...

...the ... of ...

...the ... of ...

...the ... of ...

...the ... of ...

...the ... of ...

...the ... of ...

...the ... of ...

...the ... of ...

...the ... of ...

...the ... of ...

...the ... of ...

...the ... of ...