

**DIPLOMA IN ELECTRICAL ENGINEERING
(DELVI)**

Term-End Examination

00164

June, 2017

BIEE-033 : ELECTRICAL CIRCUIT THEORY

Time : 2 hours

Maximum Marks : 70

Note : Attempt any **five** questions. Question no. 1 is **compulsory**. All questions carry equal marks. Use of scientific calculator is allowed. Assume missing data, if any.

1. Select the correct alternative :

7×2=14

- (a) At $t = 0^+$ with zero initial condition, which of the following acts as an open circuit ?
- (i) Inductor
 - (ii) Capacitor
 - (iii) Resistor
 - (iv) All of these
- (b) When a source is delivering maximum power to load, the efficiency of a circuit
- (i) is always 50%
 - (ii) depends upon circuit parameters
 - (iii) is always 75%
 - (iv) None of these

- (c) The relation between Norton's resistance (R_N) and Thevenin's resistance (R_{TH}) for a given circuit
- (i) $R_N > R_{TH}$
 - (ii) $R_N < R_{TH}$
 - (iii) $R_N = R_{TH}$
 - (iv) None of these
- (d) As per superposition theorem, the nature of the circuit is
- (i) Non-linear
 - (ii) Linear
 - (iii) Both (i) and (ii)
 - (iv) None of the above
- (e) Power factor of pure capacitor is
- (i) Unity
 - (ii) Zero
 - (iii) Infinite
 - (iv) 0.707 leading
- (f) Combined resistance value of a group of resistors connected in parallel will be
- (i) more than the largest resistor
 - (ii) more than the smallest resistor
 - (iii) less than the smallest resistor
 - (iv) between the value of the smallest and largest resistors

(g) In a circuit, a voltage of $\bar{V} = (-1 + j)$ volts produces a current of $\bar{I} = (-1 - j)$ ampere. The circuit is

- (i) Pure capacitance
- (ii) Pure inductance
- (iii) Combination of R-L
- (iv) Combination of R-C

2. (a) Find the current in the $1\ \Omega$ resistor of the network shown in Figure 1, using Thevenin's theorem.

7

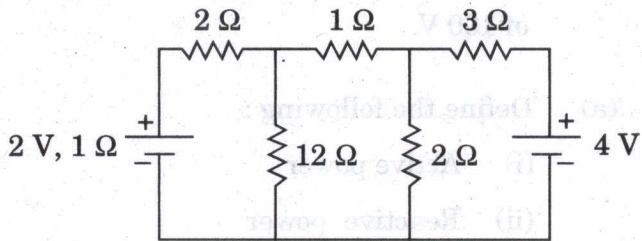


Figure 1

(b) A coil of resistance $10.05\ \Omega$ and inductance $400\ \text{mH}$ is connected in series with a $0.396\ \mu\text{F}$ capacitor. Find :

7

- (i) The resonant frequency
- (ii) Band width
- (iii) Upper and lower half-power frequencies

3. (a) Find the value of energy stored in the inductor, voltage across resistor and inductor for the circuit shown in Figure 2 under steady-state conditions. 7

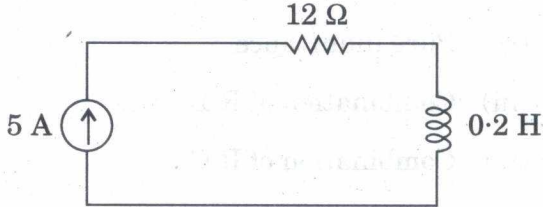


Figure 2

- (b) If a resistor dissipates energy of 250 W, find the resistance for the terminal voltage of 100 V. 7
4. (a) Define the following : 7
- (i) Active power
 - (ii) Reactive power
 - (iii) Apparent power
- (b) In a series RLC circuit, derive the expression for resonance frequency. 7
5. (a) Find the quality factor of a series RLC circuit, having resonant frequency of 10 kHz and band width of 500 Hz. 7
- (b) State Thevenin's theorem and write its limitations. 7

6. (a) Find the equivalent resistance of the circuit shown in Figure 3 along the terminals A and B.

7

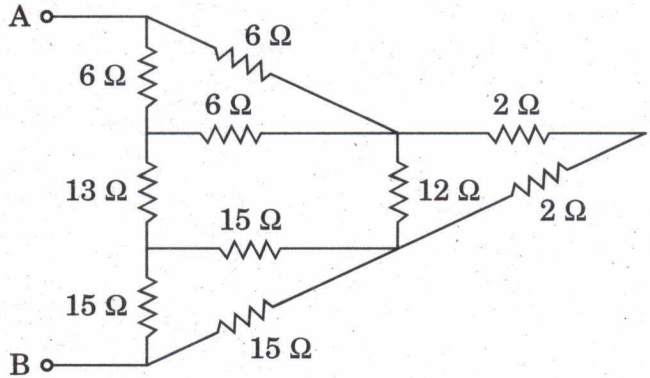


Figure 3

- (b) Explain duality of networks with suitable examples.
7. (a) Find the current in the $10\ \Omega$ resistor using superposition theorem as shown in Figure 4.

7

10

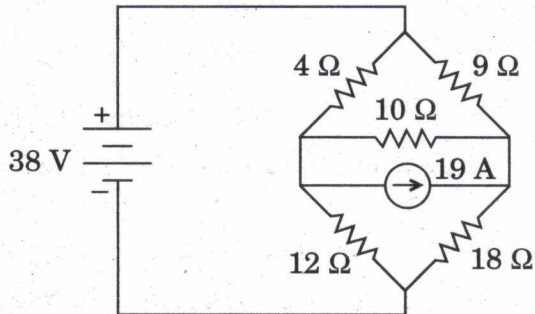


Figure 4

- (b) What do you understand by quality factor of a circuit?

4