No. of Printed Pages: 3

ET-202(B)

B.Tech. Civil (Construction Management) / B.Tech. Civil (Water Resources Engineering)

Term-End Examination

00883

June, 2018

ET-202(B): PRINCIPLES OF ELECTRICAL SCIENCES

Time: 3 hours Maximum Marks: 70

Note: Attempt any **five** questions. Use of scientific calculator is allowed. Missing data, if any, may be suitably assumed.

1. (a) Explain the following:

 $2 \times 3 \frac{1}{2} = 7$

7

- (i) Kirchhoff's current law, and
- (ii) Kirchhoff's voltage law.
- (b) Explain the maximum power transfer theorem and find out its efficiency.
- 2. (a) Explain the importance of sinusoidal signals.

 Also find the effective value and form factor. 7
 - (b) What is the three-phase system? Explain its merits over single-phase system.

ET-202(B)

1

P.T.O.

Define System. Explain and draw the block 3. (a) diagrams which represent the following systems: 7 Spring (i) R-C Network (ii) Voltage Controlled Voltage (iii) Source (VCVS) System' What is an Ideal Transformer? Explain the (b) working principle of transformer with neat diagram. 7 Explain open and short circuit test for 1-\$\phi\$ (a) 4. transformer. 7 (b) Explain the construction and working of DC Generators. 7 5. (a) Write short notes on any two of the $2 \times 3 \frac{1}{9} = 7$ following: (i) Relative merits of Analog and Digital instruments. (ii) Various interrupts 8085 in microprocessor.

(iii)

Multiplexer and its application.

	(a)	.A 3-phase, star connected alternator is rated	
`		for 5000 kVA, 50 Hz, 5 kV, 150 rpm. It has	
		negligible armature resistance and a	
		synchronous reactance $X_s = 1.5 \Omega$.	
		Find the induced emf and torque angle when	
		the machine is supplying full-load current at	
		rated voltage at (i) unity p.f; (ii) 0.8 p.f. lag.	7
6.	(a)	Explain the working of the following devices	
		with neat diagram:	7
		(i) Rectifier	
		(ii) Voltage Multiplier	
	(b)	Explain CMOS inverter with the help of its	
		characteristics.	7
7.	(a)	Explain the conversion process of the	
		following base with suitable example:	7
		(i) Binary to Hexadecimal	
	•	(ii) Hexadecimal to Binary	
		(iii) Binary to Octal	
		(iv) Octal to Hexadecimal	
,	(b)	How can you perform memory address	
		decoding? Explain with suitable example.	7