

**B.Tech. – VIEP – ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

00963

**Term-End Examination**

**June, 2018**

**BIEL-002 : ANALOG AND INTEGRATED CIRCUITS  
DESIGN**

*Time : 3 hours*

*Maximum Marks : 70*

---

**Note :** *Attempt any seven questions. All questions carry equal marks. Missing data may be suitably assumed and mentioned. Use of scientific calculators is permitted.*

---

---

1. Draw the circuit diagram of a temperature compensated logarithmic amplifier. Derive an expression for its output voltage and show it is temperature independent.  $4+4+2=10$
  
2. Explain the following applications of PLL with the help of a neatly labelled block diagram :  $5+5=10$ 
  - (a) Frequency Synthesizer
  - (b) FSK Demodulator

3. Draw the circuit diagram of a Sallen-Key VCVS second order low pass filter. Derive an expression for its transfer function and the filter parameters.  $4+6=10$
  
4. Give the circuit diagram of a triangular-wave generator and hence obtain an expression for the frequency of the output waveform.  $4+6=10$
  
5. What are comparators ? Explain the operation of an inverting comparator for positive and negative reference voltage with neatly labelled input and output waveforms.  $2+4+4=10$
  
6. What is the basic difference between an ideal and a practical integrator circuit ? Draw their circuit diagrams, their frequency response curves and the expression for their transfer functions.  $10$
  
7. Draw and explain the circuit diagram of an astable multivibrator. Derive an expression for the time-period of the output waveform.  $5+5=10$
  
8. Draw the circuit diagram of a difference amplifier using two op-amps. Derive an expression for its output voltage and gain.  $4+3+3=10$

9. Explain the advantages of active loaded differential amplifier. Draw its circuit diagram and derive its expression for voltage gain.  $3+3+4=10$

10. Write short notes on any *two* of the following :  $2 \times 5 = 10$

- (a) Instrumentation Amplifier
  - (b) Grounding and Shielding Techniques
  - (c) Sample and Hold Circuit
  - (d) F to V Converters
-