

**B.Tech. - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**00953** Term-End Examination

**June, 2018**

**BIEL-003 : DIGITAL ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

---

**Note :** Attempt any *seven* questions. Assume any missing data suitably. Use of scientific calculator is allowed.

---

---

1. (a) Convert  $(367)_8$  into Excess-3 code and Gray code. 5
- (b) Implement the expression given below with logic gates and write its complement.  
$$F (A + B) (C + D + E) (F + G + H + I).$$
 5
2. (a) Design and implement full subtractor using multiplexer. 5
- (b) Design and explain the working of a decoder. 5

3. (a) Explain the race around condition and what measures should be taken to avoid it. 5
- (b) Design a Mod-3 ripple down counter. 5
4. (a) Simplify  
 $F(A, B, C, D) = \sum (0, 2, 3, 6, 7, 8, 10, 12, 13)$   
 using K-map. 5
- (b) Derive T flip-flop from D flip-flop. 5
5. (a) Draw basic CMOS circuit and state two of its advantages. 5
- (b) Explain the working of a basic totem-pole TTL two input NAND gate. 5
6. (a) Differentiate between SRAM and DRAM. 5
- (b) Write short notes on dynamic RAM cell. 5
7. (a) Compare features of PROM, PAL and PLA. 5
- (b) Design and explain the working of DEMUX. 5
8. Design and implement conversion circuit for binary code to gray code, 10

9. (a) Differentiate between edge triggering and level triggering with proper example. 5
- (b) Write notes on the following : 5
- (i) Latches
  - (ii) Flash Memory
10. What do you mean by universal shift register ? Explain the principle of operation of 4-bit universal shift register. 10
-