

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

00703 Term-End Examination

June, 2018

BIEL-005 : ANALOG ELECTRONIC CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. All questions carry equal marks. Any missing data may be suitably assumed and mentioned. Use of scientific calculators is permitted.

1. (a) What are the h-parameters of a linear circuit? Define them. 5
- (b) A Common Emitter (CE) amplifier has the following h-parameters : $h_{ie} = 1100 \Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 25 \mu\text{S}$. If load and source resistance both are $1 \text{ k}\Omega$, find current gain and voltage gain. 5
2. (a) Describe briefly, shunt amplifier. Derive the relevant expressions. 5

- (b) Draw the series resonant circuit. Plot a curve showing the variations of circuit current with frequency and explain it briefly. 5
3. (a) The gain of an amplifier is 50 and its collector resistance $R_c = 600 \Omega$ and the input impedance $R_{in} = 1.2 \text{ k}\Omega$. Calculate overall gain when two such amplifiers are cascaded through R-C coupling. Give highlights on the results. 7
- (b) Calculate the total harmonic distortion for an output signal having fundamental amplitude of 2.5 V, second harmonic amplitude of 0.25 V, third harmonic amplitude of 0.1 V and fourth harmonic amplitude of 0.05 V. 3
4. Draw the hybrid- π model of BJT in CE connection and derive the equation for current gain. 10
5. (a) What are the various methods of cascading a two-stage transistor amplifier ? Explain their relative advantages and disadvantages. 6
- (b) Explain the operation principle of a cascode amplifier. 4

6. Draw and explain the high-frequency transistor small signal ac equivalent circuit of a BJT. Derive the expression of gain-bandwidth product (F_T). 10
7. (a) Draw the block diagram representation of an oscillator and derive the expression for Barkhausen criterion of oscillations. 5
- (b) Mention the classification of oscillators, and briefly explain each of them. 5
8. (a) Draw the circuit of an astable multivibrator. Justify that it is a two-stage RC coupled amplifier using feedback. 5
- (b) Discuss briefly the merits and demerits of RC coupled amplifier. 5
9. (a) Distinguish current feedback and voltage feedback, with appropriate circuit diagram. 5
- (b) Draw the circuit diagram of an emitter follower and explain its working principle. 3
- (c) Explain the characteristics of negative and positive feedback. 2

10. Write short notes on any *two* of the following : $2 \times 5 = 10$

- (a) Crystal Oscillator
 - (b) Wein Bridge Oscillator
 - (c) Push-Pull Amplifier
 - (d) IC-555 Timer
-