

**B.Tech. - VIEP - ELECTRICAL ENGINEERING  
(BTELVI)**

00553

**Term-End Examination**

**June, 2018**

**BIEE-014 : NETWORK THEORY**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any five questions in all. All questions carry equal marks. Assume missing data suitably. Use of scientific calculator is allowed.*

---

---

1. (a) Define a linear graph. 2
- (b) Define the following terminologies used in a network graph with suitable examples :  $4 \times 3 = 12$
- (i) Rank of a graph
  - (ii) Subgraph
  - (iii) Path
  - (iv) Co-tree

2. (a) Define incidence matrix in a graph. Also write down the properties of a tree in a graph. 7
- (b) State the Norton's theorem. Also derive the expression for Norton current ( $I_N$ ) for a two-port network. 7
3. (a) Define Reciprocity theorem and prove the theorem for suitable network. 7
- (b) Find the value of  $R_L$  in Figure 1 that results in maximum power transfer and find the maximum power delivered to load. 7

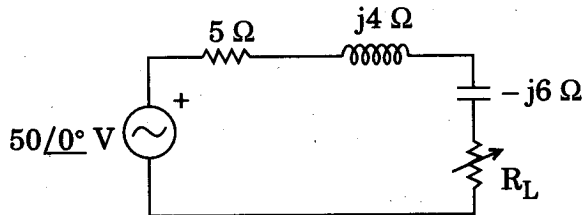


Figure 1

4. (a) State the necessary conditions for driving point function. 7
- (b) Discuss the properties of transfer function. Also state the necessary conditions for transfer function. 7
5. (a) Define the following terms : 7
- (i) Active and Passive Network
- (ii) Unilateral and Bilateral Circuits
- (b) For a two-port network, derive the Y-parameter. 7

6. (a) Derive the condition of reciprocity and symmetry in ABCD parameters. 7
- (b) A CE transistor equivalent circuit has been shown in Figure 2. Find the n-parameters. 7

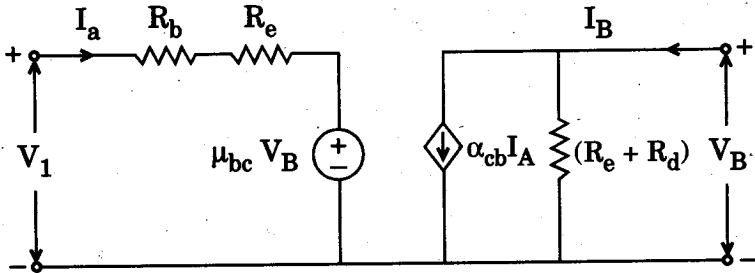


Figure 2

7. Explain in detail any **two** of the following : 2×7=14
- (a) Concept of stability of a system from pole-zero plot
- (b) Active and Passive filters
- (c) Properties of expressions of driving point immittances of LC network.