

**B.Tech. - VIEP - ELECTRICAL ENGINEERING
(BTELVI)**

00823

Term-End Examination

June, 2018

BIEE-017 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : *Attempt any seven questions. All questions carry equal marks. Missing data, if any, may be suitably assumed. Use of scientific calculator is permitted.*

1. Simplify the following using Boolean algebra : $5 \times 2 = 10$

(a) $\bar{A} + A\bar{B}C + ABC$

(b) $\bar{A}\bar{B}\bar{C} + \bar{A}BC + ABC + A\bar{B}\bar{C} + A\bar{B}C$

(c) $ABC + AB\bar{C} + A\bar{B}C$

(d) $ABCD + A\bar{B}CD + ABC\bar{D} + AB\bar{C}D + ABC\bar{D}$

(e) $\overline{A\bar{B}C + AB\bar{C}}$

2. (a) Use Karnaugh map to simplify and implement
 $F(A, B, C, D) = \sum m(0, 4, 10, 11, 14, 15)$. 5
- (b) Draw the truth table and logic circuit of the following : 5
- $$Y = AB + A + A\bar{B}C + ABC$$
3. (a) Design a full adder using half adder. 5
- (b) Implement a half subtractor using NAND gates only. 5
4. (a) What is meant by SOP and POS forms of Boolean expressions ? Give examples. 5
- (b) Reduce and find the simplified SOP form 5
- $$Y = \pi M(0, 1, 2, 3, 4, 6, 10, 11, 13)$$
5. Design a ring counter which can count '16' states. 10
6. Draw and explain the block diagram of architecture of 8086. 10
7. (a) What are the various addressing modes of 8085 ? 5
- (b) What is race-around condition in flip-flops ? How can Master-Slave JK flip-flop eliminate it ? 5
8. Design a 2-bit magnitude comparator using NAND gates only. 10

9. What are shift-registers ? Explain 'SISO' shift register in detail. 10

10. Write short notes on any *two* of the following : $2 \times 5 = 10$

- (a) Interrupts in 8085
 - (b) 'BCD' Adder
 - (c) Differences between Combinational and Sequential Circuits
-