

**DIPLOMA IN MECHANICAL ENGINEERING
(DME)**

Term-End Examination

00673

June, 2018

BEE-042 : ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : Attempt *five* questions in all. Question no. 1 is compulsory.

1. State *True* or *False* for the following statements : $7 \times 2 = 14$
- (a) A germanium atom contains two balance electrons.
 - (b) The bridge rectifier is not used for low voltage applications.
 - (c) The collector is thinner than emitter.
 - (d) The electrostatic deflection of electron in deflecting plates of a CRO is a parabola.
 - (e) A thermistor is a semiconductor device with a positive temperature coefficient of resistance.
 - (f) In the active region of operation, the MOSFET can be used as an amplifier.
 - (g) SCR is a four-junction and three-layer device.

2. (a) What is a TRIAC ? Draw and explain V-I characteristic of a TRIAC. 7
- (b) Explain the following with truth table and logic circuit : 7
- (i) Clocked SR flip-flop
- (ii) D flip-flop
3. (a) Convert the following hexadecimal numbers into decimal numbers : 7
- (i) C7F5
- (ii) 7BFC
- (b) Draw the truth table for 3-input OR and AND Gate. 7
4. (a) Draw the schematic diagram of Rotary Variable Differential Transducer and explain its working. 7
- (b) With the help of block diagram, explain the construction and working of digital voltmeter. 7
5. (a) Explain various types of single-phase AC motors with their specific applications. 7
- (b) How can transistor be used as
- (i) Amplifier, and
- (ii) Switch 7
6. Write short notes on any **two** of the following : $2 \times 7 = 14$
- (a) Clamper
- (b) UJT
- (c) Tachogenerator