

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

**00813 Term-End Examination
June, 2018**

BIELE-011 : DIGITAL SYSTEM DESIGN

Time : 3 hours

Maximum Marks : 70

*Note : Attempt any **seven** questions. All questions carry equal marks. Use of scientific calculator is allowed.*

1. Given the logic function of five variables 10
$$f(A, B, C, D, E) = (A + \overline{BC})(\overline{D + BE})$$
express the function as a sum of products. Also implement function(f) using NOR gates only.

2. (a) What is the ROM ? Give the applications of ROM and PROM. 5
(b) Explain the PLAA and FPLA programming structure. 5

3. (a) How can you differentiate 'Mealy' and 'Moore' models of sequential machines ? Explain it using structural diagram. 5
(b) Explain the principle of operation of path sensitisation method. 5

4. (a) Write an application of RS-422 in system control design. 5
- (b) Discuss the concepts and basic features of programmable system controller. 5
5. Design a 4-bit binary up-down ripple counter with D flip-flop. 10
6. What is a MSI decoder ? How can it be used for design of a system controller ? 10
7. Write short notes on any *two* of the following : $2 \times 5 = 10$
- (a) Asynchronous Finite State Machines
- (b) Hazard, Cycles and Races
- (c) MC 2900
8. Write the VHDL code for a full adder using behavioural and structural modeling. 10
9. Implement the following function with an 8 : 1 multiplexer : 10
- $$F(A, B, C, D) = \sum (0, 1, 3, 4, 8, 9, 15).$$
-