

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

00733

Term-End Examination

June, 2018

**BIELE-013 : DEVICE MODELLING FOR
CIRCUIT SIMULATION**

Time : 3 hours

Maximum Marks : 70

***Note :** Attempt any **seven** questions. All questions carry equal marks. Missing data, if any may be suitably assumed. Use of scientific calculator is permitted.*

1. Explain the principle of circuit simulation. List their advantages and disadvantages. 5+5=10
2. Explain the various models of diodes. 10
3. Write the SPICE code for a full-wave bridge rectifier circuit and simulate for its input-output characteristics. 10
4. Derive the diode current equation and mention the various SPICE parameters involved in the equation. 10

5. Explain the following models of a bipolar junction transistor : 5+5=10
- (a) Small signal
 - (b) High frequency
6. What is device scaling ? Explain short and narrow channel MOSFETs. 2+4+4=10
7. What are HBTs and HEMTs ? Briefly explain their operation. 4+6=10
8. Explain the high frequency model of a MOSFET. 10
9. Write the SPICE code for a common-source amplifier and perform its AC and Transient analysis. 10
10. Write short notes on any *two* of the following : 2×5=10
- (a) LEVEL-1 MOSFET Model
 - (b) MOS Capacitor
 - (c) Extraction of BJT model parameters
-