

**B.Tech. – VIEP – COMPUTER SCIENCE AND  
ENGINEERING (BTCSVI)**

**Term-End Examination**

00655

**June, 2019**


**BICS-009 : LOGIC DESIGN**

*Time : 3 hours*

*Maximum Marks : 70*

*Note : Attempt any seven questions. All questions carry equal marks.*

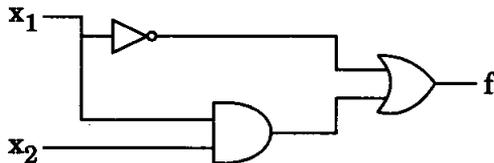1. (a) Draw the truth table for the following logic network :



Also find the boolean expression for 'f'. 2

- (b) Use boolean algebra to simplify the following boolean function : 3

$$g = \overline{\overline{(x_1 + \overline{x_2})} \cdot (\overline{x_1} + \overline{x_2})}$$

- (c) Simplify the following using K-map and draw the resulting logic diagram using AND, OR, NOT gates : 3

$$F(A, B, C, D) = \Sigma(0, 5, 6, 7, 8, 10, 11, 15)$$

- (d) What is the need of HDL ? List the basic features of any HDL. 2

2. (a) Draw the truth table and logic circuit of a 2 to 4 decoder. Construct a 3 to 8 decoder using two 2 to 4 decoders and additional gates. 5
- (b) What is the role of parity bit ? Draw the logic circuit for a 5-bit even parity generator. 5
3. (a) Add the following numbers using signed 2's complement notation. The size of number should be 8 bits. 3
- (i)  $59 + (-75)$
- (ii)  $75 + (-59)$
- (b) Draw the logic circuit of a half adder. 3
- (c) Explain the adder/subtractor unit with the help of a diagram. 4
4. (a) Draw the logic circuit truth table and graphical symbol of clocked T-flip-flop. Explain the logic circuit of this flip-flop. 5
- (b) What are master-slave flip-flops ? Why are they needed ? 3
- (c) Differentiate between combinational and sequential circuits. 2
5. (a) Explain the working of a 3-bit shift register, with the help of a diagram. Also show a sample sequence of shift of values through this register. 6
- (b) Differentiate between registers and counters. Can a counter be made using D-flip-flop ? Justify your answer. 4

6. (a) Explain the use of state transition diagram with the help of an example/diagram. 4
- (b) List the steps of design of a sequential circuit. 4
- (c) What is meant by "edge-triggered flip-flops" ? 2
7. What is the need of Analog to Digital Converter ? Explain with the help of an example. What are the basic performance issues for this conversion ? Explain the terms accuracy and resolution in this context. List the techniques of Analog to Digital conversion. 10
8. Explain the characteristics of TTL circuits. List their advantages and disadvantages. Explain a fundamental TTL gate with the help of a diagram. 10
9. Differentiate between the following :  $5 \times 2 = 10$
- (a) Minterm and Maxterm
- (b) Encoder and Decoder
- (c) Signed 1's complement and Signed 2's complement notation of binary numbers
- (d) T-flip-flop and D-flip-flop
- (e) Serial and Parallel input to a register

**10. Define the use of the following in the context of digital design (any *five*) :** **5×2=10**

- (a) Don't care condition
  - (b) BCD
  - (c) Read-only memory
  - (d) Logic probe
  - (e) Fixed point numbers
  - (f) Decade counter
  - (g) Digital clock
  - (h) Programmable logic array
-