

B.Tech. (BTCSVI / BTECVI / BTELVI)

Term-End Examination

June, 2019

00575

**BIEL-001 : BASICS OF ELECTRONICS
ENGINEERING**

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. All questions carry equal marks.

1. (a) Draw the energy band diagram of metal insulator and semiconductor. 5
- (b) Explain the generation of holes and electrons in an intrinsic semiconductor. 5
2. (a) What is Fermi level ? Where does it lie in N type and P type semiconductors ? 5
- (b) How does Avalanche breakdown differ from Zener breakdown ? 5

3. Explain any *two* of the following : 2×5=10
- (a) Tunnel Diode
 - (b) Photodiode
 - (c) LED
4. Explain the construction and working of NPN transistor. 10
5. Explain the formation of barrier potential in an open circuit PN junction diode. Also derive the expression for potential barrier. 10
6. What is full-wave rectifier ? Derive the expression for rectifier efficiency and ripple factor. 10
7. (a) Draw the circuit of common base transistor and explain its input output characteristics. 5
- (b) Explain the Hall effect. List the applications of Hall effect. 5
8. (a) Explain the working of capacitor filter and inductor filter. 5
- (b) Explain voltage regulation in series regulator. List the applications of voltage regulator. 5

9. Explain any *two* of the following : 2×5=10

(a) FET

(b) MOSFET

(c) Miller Theorem

10. Compare CE, CB and CC configurations of a transistor. Draw I – V characteristics of each configuration. Also explain transit time effect. 10
