

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

June, 2019

00525

**BIEL-002 : ANALOG AND INTEGRATED CIRCUITS
DESIGN**

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. All questions carry equal marks. Missing data may be suitably assumed and mentioned.

1. Draw and explain the circuit diagram of an instrumentation amplifier with its advantages in detail. $4+4+2=10$
2. Explain the importance of DC level shifter stage used in Op-Amp. Draw and discuss the working principle of voltage to frequency (V to F) converter with neat circuit diagram. $4+6=10$

3. Explain the significance of filter order in filter design. Draw the circuit diagram of Sallen-Key VCVS second order low pass filter with its specifications. Derive an expression for its transfer function. $2+4+4=10$

4. What are the ideal characteristics of an Op-Amp ? Draw and explain the circuit diagram of a Schmitt trigger with its waveforms. $4+6=10$

5. Draw and explain the circuit diagram of a monostable multivibrator. Derive an expression for the time-period of the output waveform. $6+4=10$

6. Explain the concept of virtual ground in Op-Amp. Draw and explain the circuit diagram of a Precision rectifier with its waveforms. $4+6=10$

7. Explain the application of Phase Locked Loop (PLL) in AM demodulator with a labelled block diagram in detail. 10

8. Analyse the operation of a differential amplifier with active load. What is the effect of parameter mismatch on the gain of differential amplifier ? $6+4=10$

9. Draw voltage current feedback amplifier. Draw the basic amplifier without feedback and derive open loop transfer gain and from this find the closed loop transfer gain. 10
10. Write short notes on any *two* of the following : 2×5=10
- (a) Log Amplifier
 - (b) Current to Voltage (I-to-V) Converter
 - (c) Current Mirror Circuit
-