

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

00525

Term-End Examination

June, 2019

BIEL-003 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. Assume any missing data suitably. Use of scientific calculator is allowed.

1. (a) Show that 5

$$AB'C + B + BD' + ABD' + A'C = B + C.$$

(b) Express the Boolean function $F = AB + A'C$ in a product of Maxterm. 5

2. Reduce the expression in SOP and POS form using K-map. 10

$$F(A, B, C, D) = \sum_m(1, 5, 6, 12, 13, 14) + d(2, 4)$$

3. Explain carry look ahead adder with neat diagram and relevant expressions. 10

4. (a) Explain briefly 3 to 8 line decoder. 4

 (b) What is multiplexer ? Explain the working of 4 to 1 line multiplexer with logic circuit and function table. 6

5. Explain the working of master slave JK flip-flop with the help of a logic diagram, function table, logic symbol and timing diagram. 10

6. Describe the working principle of universal shift register with the help of logic diagram and mode control table. 10

7. Design a synchronous Mod-6 counter using clocked T flip-flop. 10

8. (a) Explain the operation of tri-state TTL NAND gate with the help of a neat diagram. 8

 (b) List the two advantages of Totem-pole output arrangement. 2

9. (a) Compare the characteristics of TTL, ECL, RTL and CMOS. 7
- (b) Define the following characteristics of digital ICs : 3
- (i) Power dissipation
 - (ii) Noise margin

10. Write short notes on *any two* of the following : 2×5=10

- (a) Static and Dynamic RAM Cell
 - (b) EPROM
 - (c) ASCII Codes
-