

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

June, 2019

00675

BIEL-005 : ANALOG ELECTRONIC CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : (i) Attempt any seven questions.

(ii) Any missing data may be suitably assumed and mentioned.

(iii) Use of scientific calculators is permitted.

-
-
1. (a) Explain equivalent circuit of BJT using h-parameters for CC configuration. 5
(b) Discuss the effect of cascading on an amplifier. 5
 2. (a) Describe high frequency model for CE configuration. 5
(b) Discuss about series resonance. 5
 3. (a) Explain Darlington configuration with circuit diagram. 5
(b) If two transistors having $\beta_1 = 50$ and $\beta_2 = 40$ are connected as Darlington pair then calculate net β . 5

- | | | | |
|-----|-----|--|----|
| 4. | (a) | Discuss class-C amplifier operation. | 5 |
| | (b) | Explain Barkhausen criterion of oscillation and classify oscillators. | 5 |
| 5. | (a) | Calculate frequency of oscillation for wein bridge oscillator if $R = 4 \text{ k}\Omega$ and $C = 0.25 \text{ }\mu\text{F}$. | 5 |
| | (b) | Discuss the merits and demerits of negative feedback amplifier. | 5 |
| 6. | | Explain Hartley oscillator and derive expression for resonant frequency. | 10 |
| 7. | | Draw the circuit diagram of Push-pull amplifier and explain its working principle. | 10 |
| 8. | (a) | Mention the applications of astable, monostable and bistable multivibrators. | 5 |
| | (b) | Draw and explain the circuit diagram of monostable multivibrator. | 5 |
| 9. | (a) | Compare different transistor amplifier configuration. | 5 |
| | (b) | An amplifier has output voltage of 40 V and 8% harmonic distortion when input voltage is 0.05 V. If 2.5% of output is mixed with input in phase opposition, then calculate output voltage and harmonic distortion. | 5 |
| 10. | | Write short notes on any two of the following : $2 \times 5 = 10$ | |
| | (a) | Advantages and disadvantages of tuned amplifier. | |
| | (b) | Frequency stability of oscillatory circuits. | |
| | (c) | UJT | |
| | (d) | High frequency response of BJT. | |
