


BTCSEVI / BTECVI / BTELVI**Term-End Examination, 2019****BIEE-001 : BASICS OF ELECTRICAL ENGINEERING**

Time : 3 Hours]


[Maximum Marks : 70

Note : Answer any seven questions in all. All questions carry equal marks. Use of Scientific Calculator is allowed.

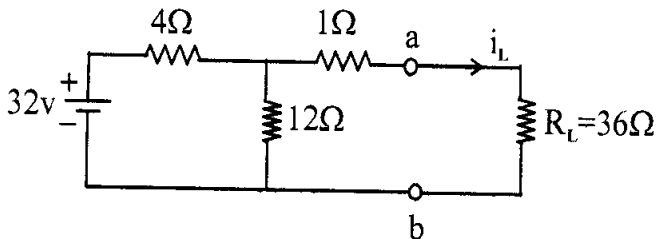1. State Thevenin Theorem. Find the current (i_L) and thevenin equivalent circuit of the circuit to the left of the terminal a - b. [3+7=10]



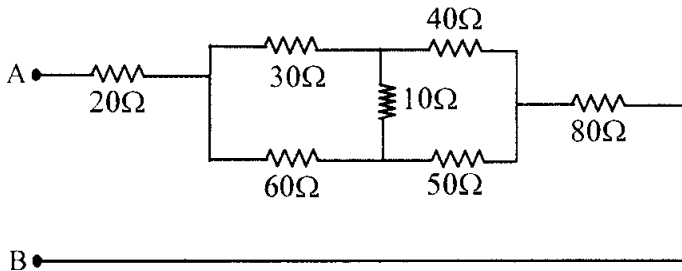2. (a) In the network shown below, determine resistance between A and B. [5]



(b) What do you understand by temperature coefficient of resistance ? Give the name of 3 material whose resistance decrease with rise in temperature. [5]

3. (a) Explain the terms (**any two**) : [5]

(i) Magnetic intensity


(ii) Magnetic flux density

(iii) Permeability


(b) Explain the phenomenon of force between two parallel current carrying conductors. [5]

4. (a) Explain Fleming's Left and Right hand rules with the help of neat diagram. Where are they applied ? [5]

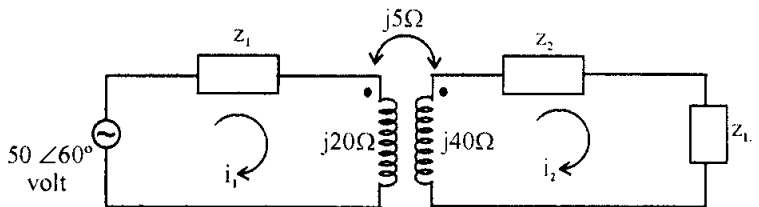- (b) Explain the Super Position theorem with suitable examples. [5]
5. (a) Derive an expression for rise and decay of current in a R-L circuit. [5]
- (b) Derive the conversion of Delta to Star network. [5]
6. State "Blondel Theorem". Explain two and three wattmeter method to measure power in three phase unbalanced load. [10]
7. Define Power Factor. What are the drawbacks of low power factor ? Also discuss the importance of power factor. [10]
8. (a) In the circuit, calculate the input impedance and current I_1 , take $z_1 = 60 - j100\Omega$, $z_2 = 30 + j40$ and $z_L = 80 + j60\Omega$. [7]



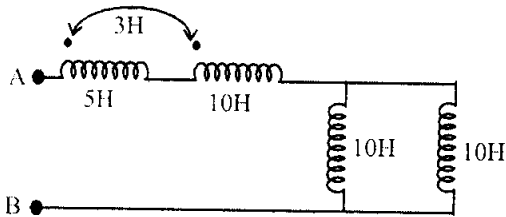- (b) Find the equivalent inductance of the circuit across terminal A - B. [3]



9. Write short notes on any two of the following : [2×5=10]
- (a) Hysteresis loop
 - (b) Nickel cadmium cell
 - (c) Impedance triangle

----- X -----