

**B.Tech. - VIEP - ELECTRICAL ENGINEERING
(BTELVI)**

Term-End Examination

00525

June, 2019

BIEE-014 : NETWORK THEORY


Time : 3 hours

Maximum Marks : 70

Note : Attempt any five questions. All questions carry equal marks. Use of scientific calculator is allowed.

1. (a) In graph theory, determine the relation between Branch voltage matrix $[V_b]$, Twig voltage matrix $[V_T]$ and Node voltage matrix $[V_n]$. 7
- (b) Define the following terms with an example of each : 7
- (i) Fundamental tie set matrix
- (ii) Planar and Non-planar graph

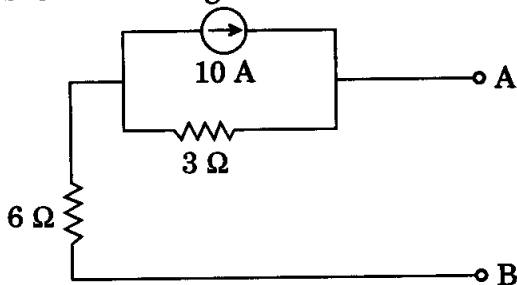2. (a) State and prove Tellegen's theorem. 7
- (b) What are the values of Norton's equivalent current source (I_N) and equivalent resistance (R_N) across the load terminal of the circuit shown in the figure below? 7



3. (a) How can stability of the network be obtained with the help of pole-zero plot? 7
- (b) Explain various properties and necessary conditions for transfer functions. 7
4. (a) Show that when two networks N_1 and N_2 are connected in series, the equivalent z-parameters of combined network is the sum of z-parameters of each individual two-port network. 7
- (b) The currents I_1 and I_2 at the input port and the output port respectively of a two-port network are given by

$$I_1 = 6V_1 - V_2 \text{ and } I_2 = -V_1 + 2V_2.$$

Find the equivalent π -network, and the input impedance when a load of $(4 + j7)$ ohm is connected across the output port. 7

5. (a) Synthesize the function

$$z(s) = \frac{s(s^2 + 12)}{(s^2 + 2)(s^2 + 20)}$$

using the Foster form-II.

7

- (b) Check whether the polynomial

$s^4 + s^3 + 7s^2 + 4s + 6$ is Hurwitz or not.

7

6. (a) Discuss the general characteristics of a Low Pass filter.

7

- (b) What are the limitations of passive filters ?
Draw the schematic diagram of a High Pass filter.

7

7. Write short notes on any *two* of the following :

$2 \times 7 = 14$

- (a) Reciprocity Theorem
(b) Transform Impedance Function
(c) Interconnection of Two-port Network
-