

1256845

No. of Printed Pages : 3

BIEE-017

**B. TECH. VIEP-ELECTRICAL
ENGINEERING (BTELVI)**

Term-End Examination

June, 2019

BIEE-017 : DIGITAL ELECTRONICS

Time : 3 Hours

Maximum Marks : 70

Note : Attempt any seven questions. All questions carry equal marks. Missing data, if any, may be suitably assumed. Use of scientific calculator is allowed.

1. Simplify the following using Boolean algebra :

$2\frac{1}{2}$ each

(a) $AB + \overline{A}BC + B\overline{C} = AC + B\overline{C}$

(b) $\overline{A}BC + B + B\overline{D} + AB\overline{D} + \overline{A}C = B + C$

(c) $A [B + \overline{C} (\overline{AB} + \overline{AC})]$

(d) $\overline{(A + BC)} (\overline{A}B + ABC)$

2. (a) Reduce the expression $f = \Sigma m (0, 2, 3, 4, 5, 6)$ using mapping and implement it in NAND logic. 5

(A-39) P. T. O.

- (b) Minimize the output function : 5

$$f_1 = \Sigma m (0, 2, 6, 10, 11, 12, 13)$$

$$+ d (3, 4, 5, 14, 15)$$

$$\text{and } f_2 = \Sigma m (1, 2, 6, 7, 8, 13, 14, 15)$$

$$+ d (3, 5, 12)$$

3. (a) Realize a full-subtractor using NAND gate only. 5
- (b) Implement the function $F(a, b, c) = ab + \bar{b}c$ using 4 : 1 MUX. 5
4. (a) With the help of a gate level logic diagram and a truth table. Explain decimal to BCD encoder. 5
- (b) Implement the function F with two level forms AND-NOR : 5
- $$F(A, B, C, D) = \Sigma m (0, 1, 2, 3, 4, 8, 9, 12)$$
5. (a) For what minimum value of propagation delay in each flip-flop will a 10 bit ripple counter skip a count when it is clocked at 10 MHz. 5
- (b) Design a synchronous 3-bit down counter using J-K flip-flop. 5
6. Draw and explain the architecture of 8086 microprocessor. 10

7. Write short notes on any *two* of the followings : 5 each
- (i) Synchronous and Asynchronous counter
 - (ii) Programmable Logic Array (PLA)
 - (iii) Race round condition in flip-flop
8. Explain the following terms : 2 each
- (i) Propagation delay time
 - (ii) Setup time
 - (iii) Power dissipation
 - (iv) Pulse width
 - (v) Hold time
9. With the help of diagrams, explain the working of 4-bit universal shift registers. 10
10. Explain the interrupts and flags in 8085 microprocessors. 10