

**B.Tech. MECHANICAL ENGINEERING  
(COMPUTER INTEGRATED  
MANUFACTURING) /  
B.Tech. (AEROSPACE ENGINEERING) (BTAE)  
Term-End Examination**

00602

June, 2019

**BME-021 : PRINCIPLES OF ELECTRICAL AND  
ELECTRONICS SCIENCE**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Question no. 1 is compulsory. Answer any two questions from Section A and any two from Section B. Use of scientific calculator is allowed.*

---

1. State whether the following statements are *True* or *False* :

$7 \times 2 = 14$

- (a) An electrical network with 6 independent nodes will have 5 loop equations.
- (b) The reluctance of a material is defined as its ability to conduct magnetic flux.
- (c) The average value of the alternating quantity is more than the rms value.

- (d) The eddy current losses in the transformer occur in the core.
- (e) At start, the slip of the induction motor is zero.
- (f) The emitter of a transistor is doped heavily.
- (g) The most commonly used transistor circuit arrangement is common emitter.

## SECTION A

Attempt any **two** questions from this section.

2. (a) What are the factors affecting the resistance of a conductor ? How do they affect its value ? 7
- (b) State and explain Kirchhoff's current and voltage laws. 7
3. (a) A flux density of  $1.2 \text{ Wb/m}^2$  is required in the 2 mm air gap of an electromagnet having an iron path 1 metre long. Calculate the magnetising force and current required if the electromagnet has 1273 turns. Assume relative permeability of iron is to be 1500. 7
- (b) Give the comparison between STAR and Delta connected systems. 7
4. Write short notes on the following :  $4 \times 3 \frac{1}{2} = 14$
- (a) Torque-slip Characteristics of Induction Motor
- (b) OC and SC Tests of Transformer
- (c) Single-phase Induction Motor
- (b) AC Servomotor

## SECTION B

*Attempt any two questions from this section.*

5. (a) Draw the symbol, structure and equivalent circuit of TRIAC and IGBT. 7
- (b) Draw the circuit diagram of Common-Emitter Amplifier and also derive the expression for the voltage gain. 7
6. (a) State and explain the De Morgan's theorem with diagrams. 7
- (b) Draw the TTL NAND Gate circuit and also explain its operation. 7
7. (a) What is the difference between volatile and non-volatile memory? 7
- (b) What are the various registers in 8085? Name the 16 bit registers. 7
-