

00545

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)**

Term-End Examination

June, 2019

BIELE-004 : RF CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : (i) Attempt any seven questions.

(ii) Missing data may be suitably assumed.

(iii) All questions carry equal marks.

1. (a) Explain IEEE frequency spectrum on the basis of frequency band, frequency and wavelength. 5
- (b) Compute the intrinsic wave impedance, phase velocity and wavelengths of an electromagnetic wave in free space for the frequencies $f=30$ MHz, & 300 MHz. 5
2. (a) What is High Frequency Inductor ? Draw electric equivalent circuit representation for a high frequency wire wound inductor. 5
- (b) Give two examples of Transmission lines with suitable diagram and field distribution. 5
3. Derive General transmission line voltage and current equation. 10

4. (a) Discuss noise models for active and passive components. 5
(b) Define basic voltage and current definition for single and multiple network. 5
5. (a) Explain characteristics of RF amplifier with the help of block diagram. 5
(b) Explain stabilization method for RF BJT amplifier. 5
6. (a) Explain basic oscillator model with the help of Barkhausen Criterion. 5
(b) Explain feedback oscillator design on the basis of T-type feedback. 5
7. Explain Voltage Controlled Oscillator and derive the equation of resonance frequency. 10
8. (a) Discuss low noise amplifier topologies. 5
(b) What is the role of negative resistance in oscillator ? 5
9. Write short notes on **any two** of the following : 5+5=10
(a) Frequency synthesizers
(b) Class AB power amplifier
(c) Resonators
10. Define voltage reflection coefficient, and derive the equation of voltage reflection coefficient for a terminated lossless transmission line. 10
-