

No. of Printed Pages : 3

BIELE-012

**B. Tech. VIEP ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination**June, 2019****BIELE-012 : ELECTRONIC SWITCHING CIRCUITS***Time : 3 Hours**Maximum Marks : 70*

Note : Attempt any seven questions. All questions carry equal marks. Assume missing data, if any. Use of scientific calculator is permitted.

1. What is the difference between a Latch and a Flip-Flop ? Explain with the neat sketch, the operation of a SR flip-flop and a J-K flip-flop. 10
2. Design a 3-bit up counter with the help of J-K flip-flop. 10
3. What is Combinational Network ? Explain all the steps for designing a hazard free combinational network. 10

(A-7) P. T. O.

4. With the help of suitable example, explain the synthesis of symmetric functions. 10
5. Write short notes on any *two* of the following :
5 each
- (a) Shift Register
 - (b) Sequence Detector
 - (c) Conversion of Mealy circuit to Moore circuit
6. (a) Write down the difference among a truth table, a state table and an excitation table with suitable examples. 5
- (b) What do you mean by GLITCH and propagation delay in asynchronous counters ? 5
7. Derive the equation for a characteristic impedance of symmetrical T and π -networks. 10
8. (a) Explain the working principle of negative edge triggered D flip-flop. 5
- (b) How can you differentiate the architecture of an asynchronous up counter and down counter ? 5

[3]

9. (a) Explain dynamic hazards with suitable example. 5
- (b) Explain pulse mode sequential circuit. 5
10. Design a contact network with 4 inputs relay W, X, Y and Z, which receives BCD numbers and produces a signal whenever the present numbers is 03 or multiple of 03. 10