

00585

No. of Printed Pages : 2

BIEEE-016

B.Tech. - VIEP - ELECTRICAL ENGINEERING

(BTELVI)

Term-End Examination, 2019

BIEEE-016 : INDUSTRIAL DRIVES

Time : 3 Hours]

[Maximum Marks : 70

Note : Attempt any seven questions. All questions carry equal marks. Use of scientific calculator is permitted. Missing data, if any, may be suitably assumed.

1. What are the advantage of Electrical drives ? State the essential parts of electrical drives. What are the functions of a power modular ? [10]
2. What do you mean by "Load Equalization" ? Why is flywheel not used with a synchronous motor for load equalization ? Is it possible to apply load equalization for reversible drives ? Discuss. [10]
3. Describe the operation of closed-loop torque control scheme and it's application. [10]

4. A 220 V, d.c. shunt motor takes 50 A, when giving its rated output at 1500 rpm, its total resistance is 0.25Ω . Determine the resistance to be added in series with the motor to obtain the rated torque at a) starting b) 1000 RPM. [10]
5. (a) Explain the speed control of a dc motor with the help of a chopper. [5]
- (b) Explain Slip power recovery scheme for 3-phase induction motor drive. [5]
6. With a suitable example of a motor driving a hoist load, Explain the speed Torque convention for four Quadrant operation of an Electric drive. [10]
7. Explain the working of Solar and Battery powered drives. [10]
8. Explain the 120° 'OR' 180° degree mode of operation of Voltage source inverter. [10]
9. Explain the Brushless dc motor for servo application. [10]

----- X -----